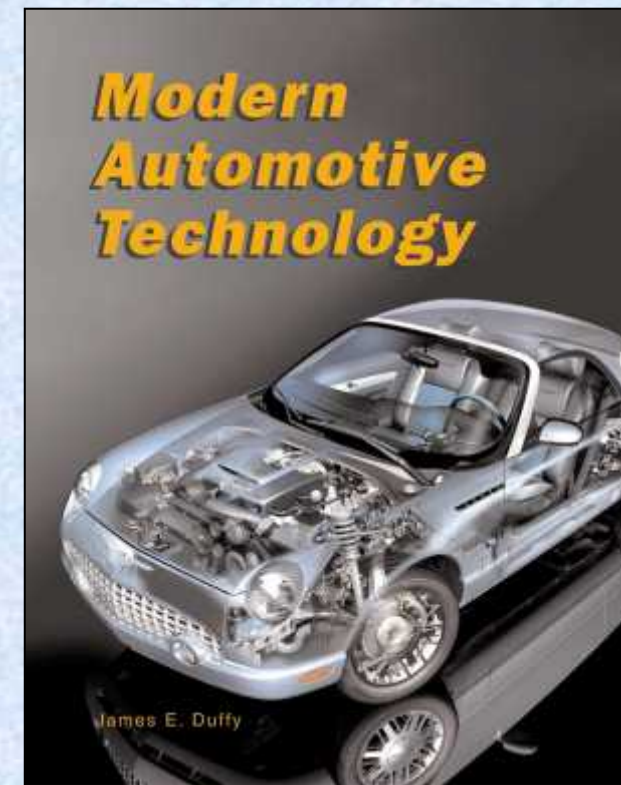


powerpoint for

# Modern Automotive Technology

by  
**Russell Krick**



Publisher  
**The Goodheart-Willcox Co., Inc.**  
Tinley Park, Illinois

# Chapter 31

## Starting System Fundamentals

# Contents


- ❑ Starting system principles
- ❑ Starting motor construction

# Starting System Principles

The starting system uses battery power and an electric motor to turn the engine crankshaft for engine starting
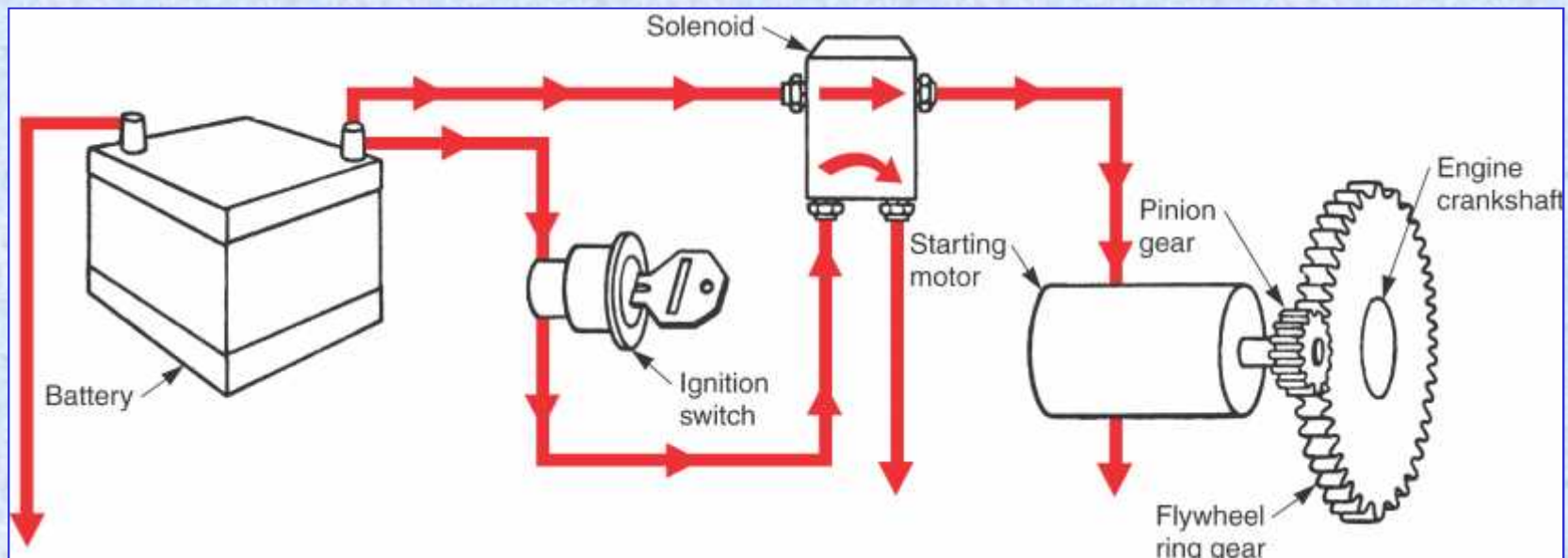
# Basic Starting System

- ❑ The ignition switch energizes the solenoid
- ❑ The solenoid energizes the starting motor



# Components

- ❑ Battery
  - source of energy
- ❑ Ignition switch
  - allows driver to control operation
- ❑ Solenoid
  - high current relay (switch)
- ❑ Starting motor
  - high torque electric motor

# Starting System Energized

- ❑ With the ignition key in the “start” position, current flows through the solenoid coil
- ❑ Magnetism closes the solenoid contacts, connecting the battery to the starting motor
- ❑ The motor turns the flywheel ring gear

# Starting System De-energized

- ❑ With the ignition key released to the “run” position, no current flows to the solenoid coil
- ❑ The solenoid contacts open, the starter stops turning, and the starter gear moves away from the flywheel




# Starting Motor Fundamentals

- ❑ Converts electrical energy from the battery to mechanical energy to crank the engine
- ❑ Produces a turning force through the interaction of magnetic fields inside the motor assembly

# Magnetic Field Action


- ❑ Made up of invisible lines of force
- ❑ Since like charges (fields) repel each other and unlike charges (fields) attract each other, magnetic fields can produce motion

# Magnetic Field Action

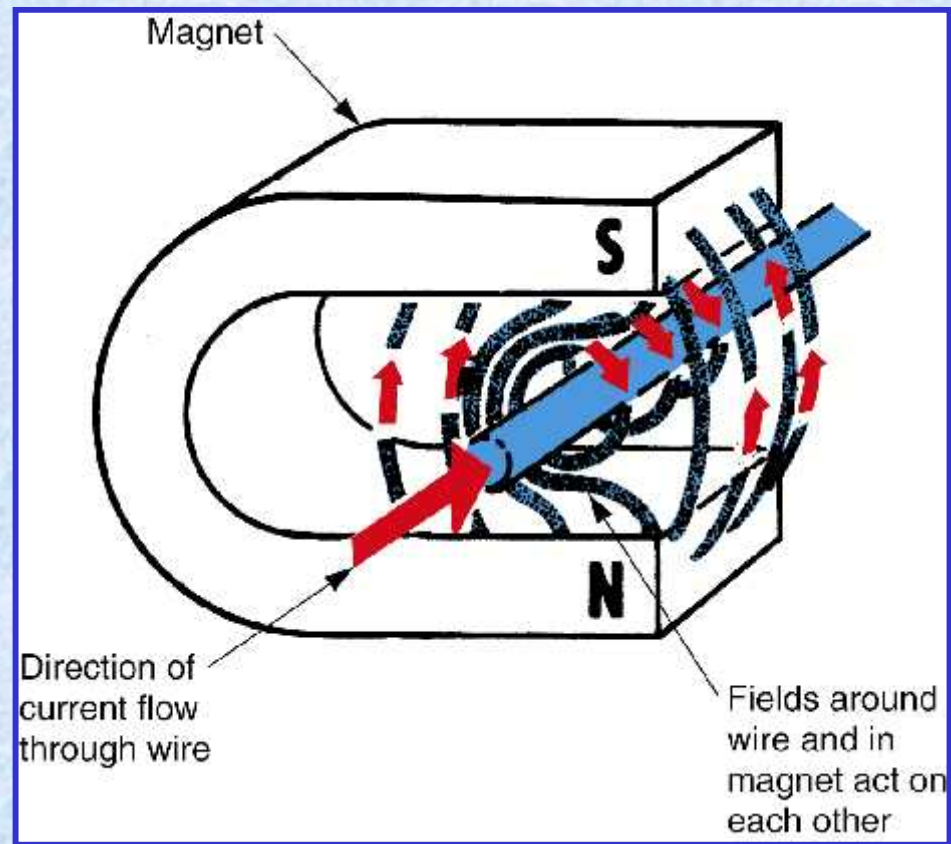
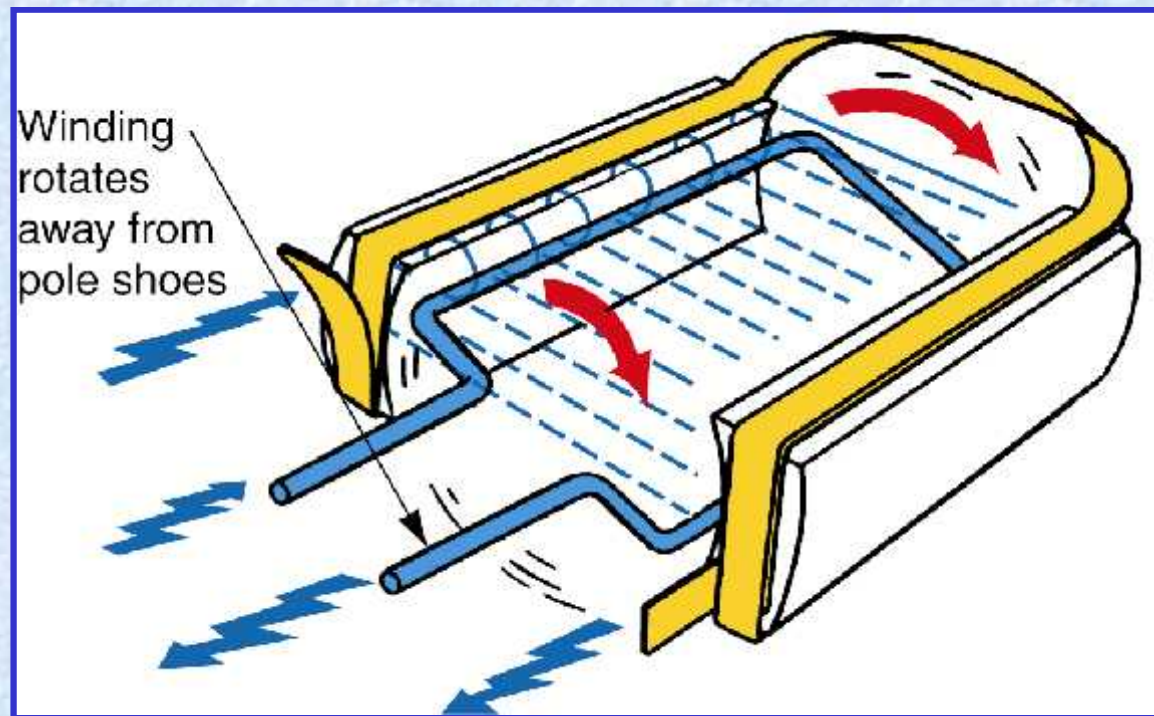
# Simple Electric Motor

If a current-carrying winding is placed inside a magnetic field, the winding rotates away from the pole shoes




# Commutator and Brushes

- ❑ Keep a motor turning by controlling the current through the windings
- ❑ Together, they serve as a sliding contact between battery power and the windings
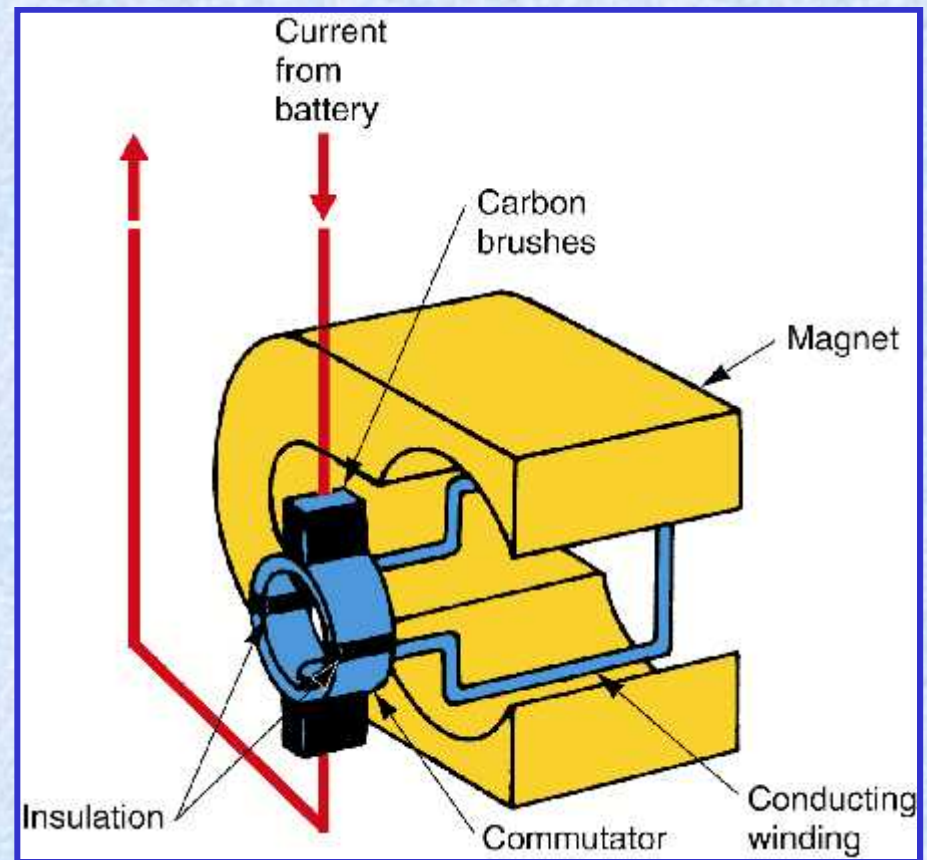
# Commutator and Brushes

The commutator reverses the electrical connection when the loop rotates around



# Increasing Motor Power

- ❑ Several windings (loops of wire) and a commutator with many segments are used to increase motor power
- ❑ As the motor spins, many windings contribute to the motion

# Armature


- ❑ Supports the windings
- ❑ Increases the strength of each winding's magnetic field



# Field Windings

- ❑ Stationary insulated wire wrapped in a circular shape
- ❑ When current flows, the magnetic field between the pole shoes becomes very large
- ❑ This field acts against the armature's field, producing motion

# Armature and Field Windings

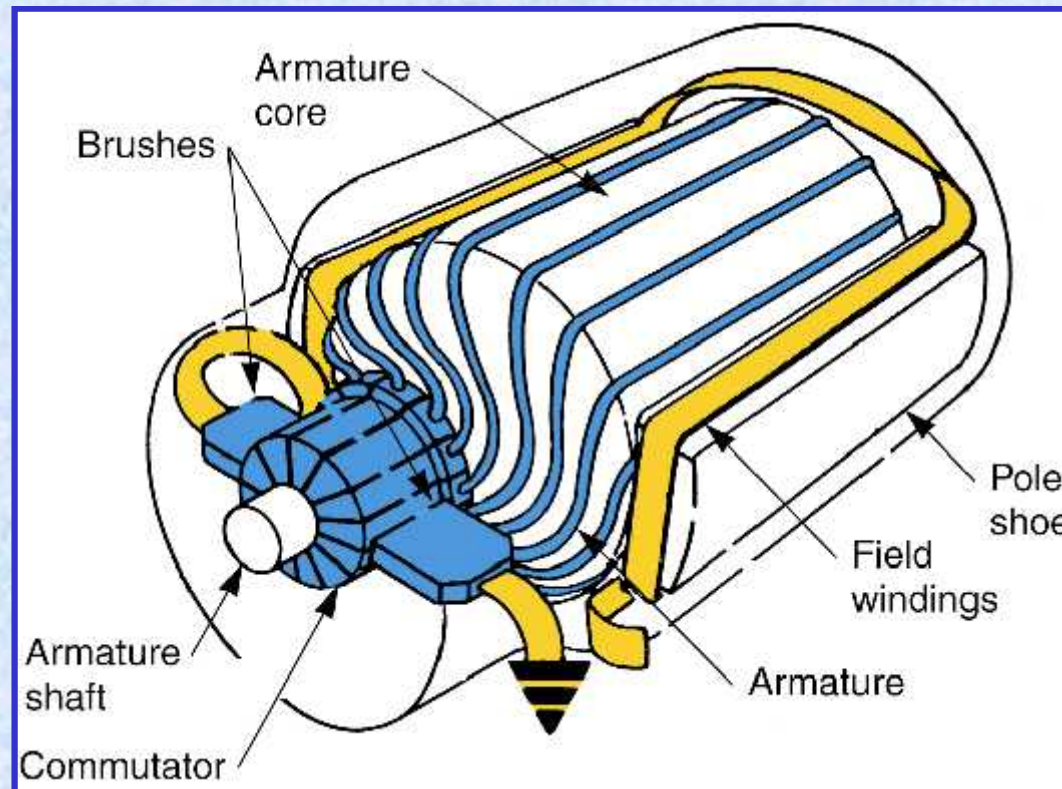


# Starter Pinion Gear

- ❑ Small gear on the armature shaft
- ❑ Engages a large ring gear on the engine flywheel
- ❑ Moves into and meshes with the flywheel ring gear

# Starter Pinion Gear

Part of the pinion drive mechanism

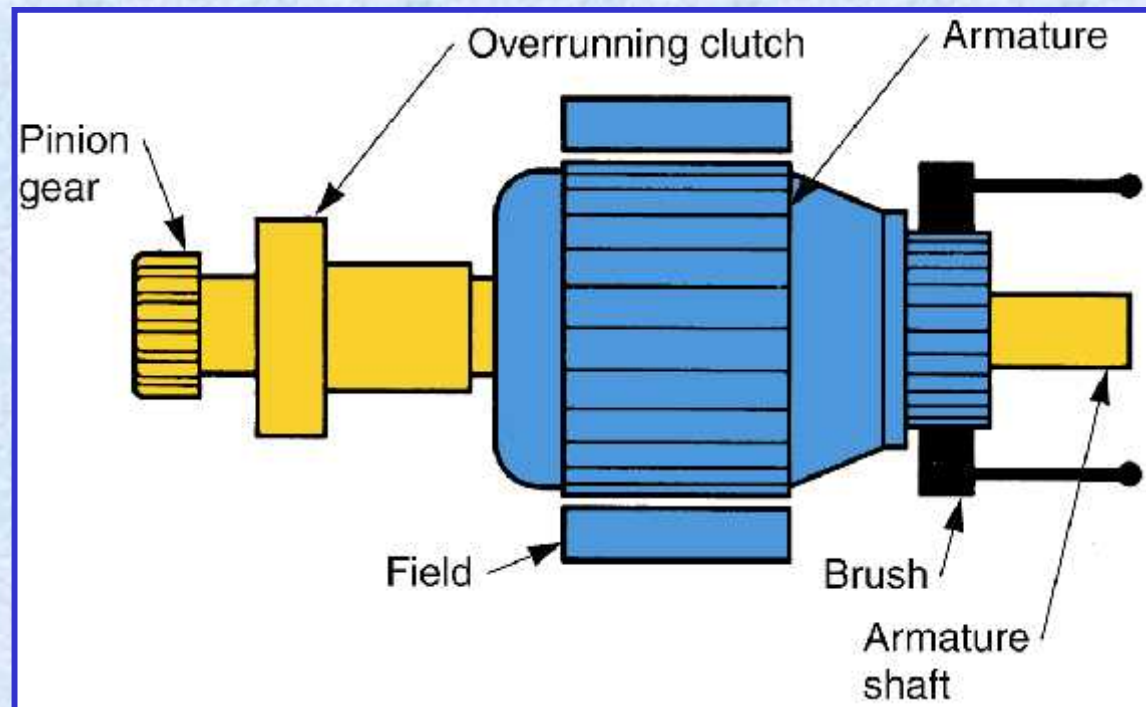


# Overrunning Clutch

- Locks in one direction
- Releases in the other direction
- Allows the pinion gear to turn the flywheel ring gear for starting
- Lets the pinion gear freewheel when the engine starts

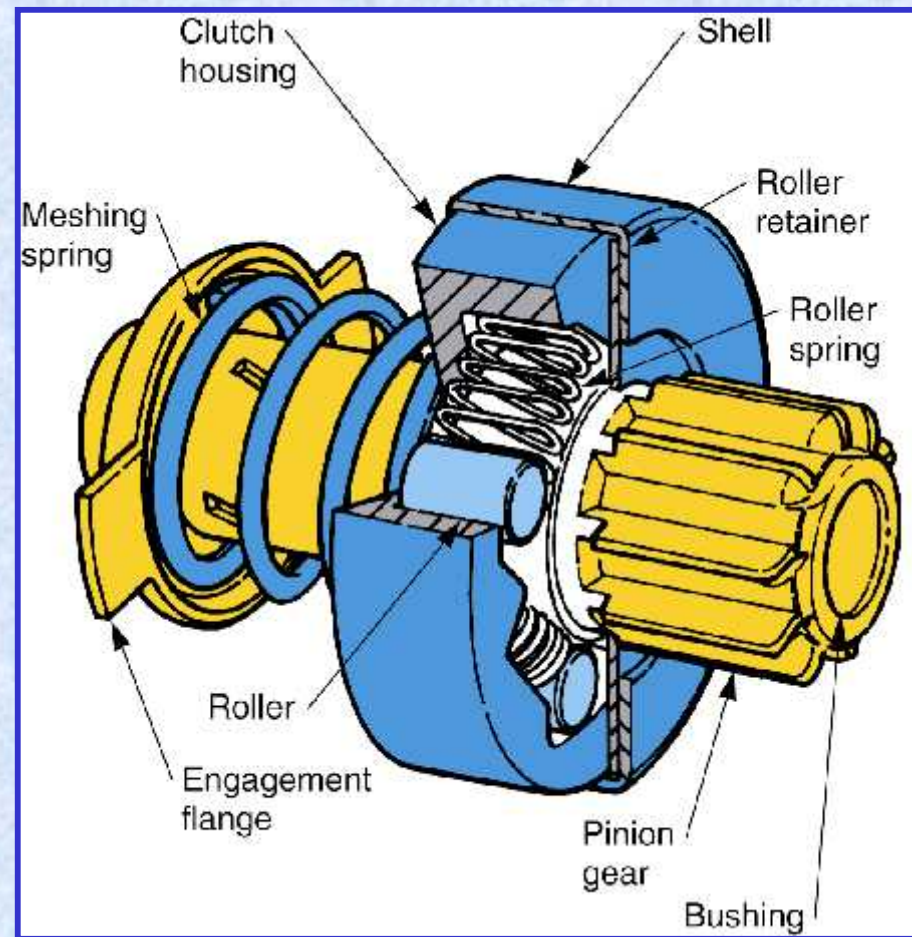
# Overrunning Clutch

Locks the flange to the pinion gear in one direction and releases in the other direction



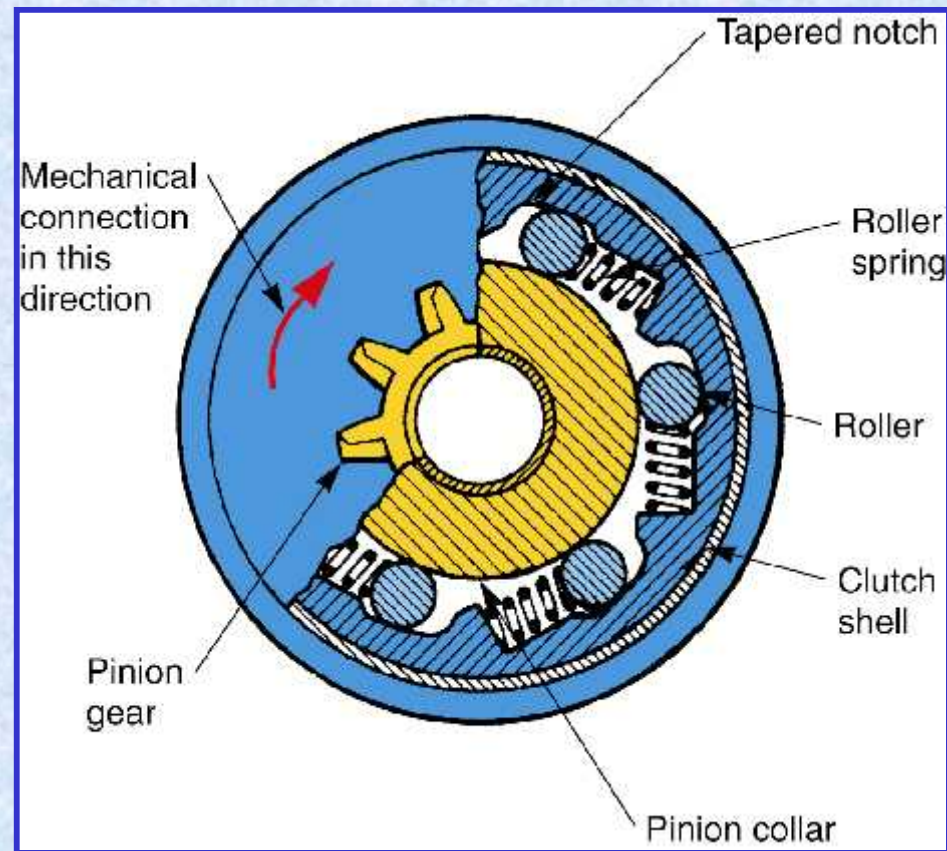
# Overrunning Clutch Operation

Rollers jam and lock in one direction and release in the other direction


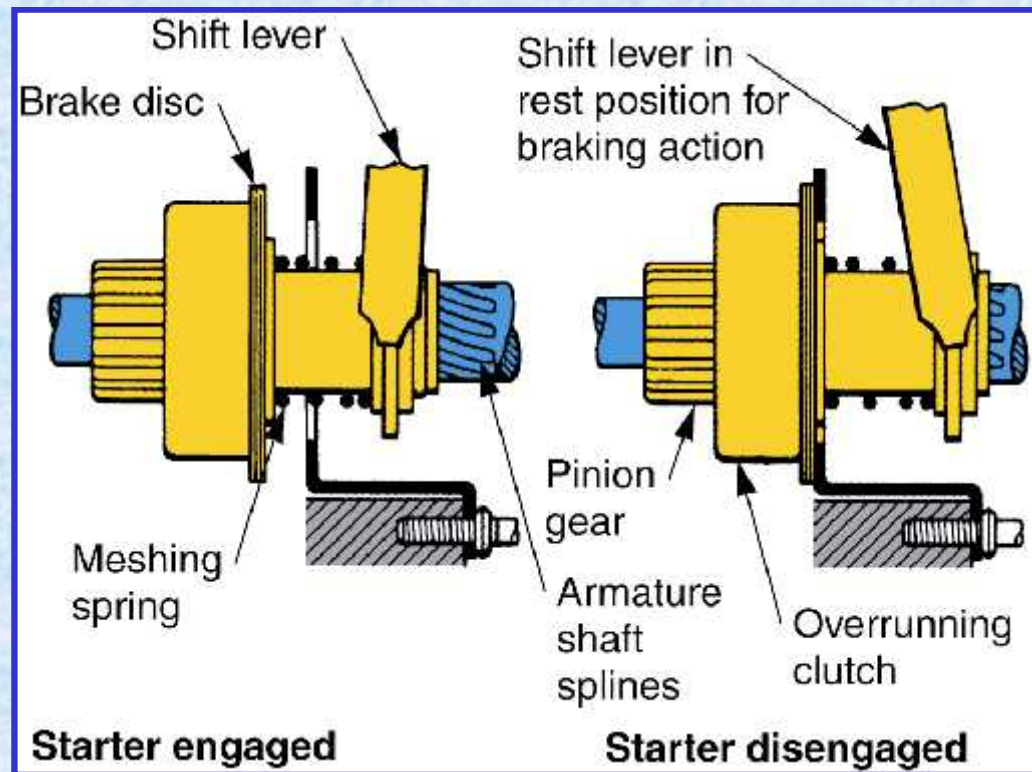
# Pinion Gear Assembly

Pinion gear assembly slides on the shaft for engagement






# Starter Solenoid

- ❑ An electromagnetic switch
- ❑ Makes an electrical connection between the battery and the starting motor
- ❑ Allows the low current ignition switch circuit to control the high current starting motor
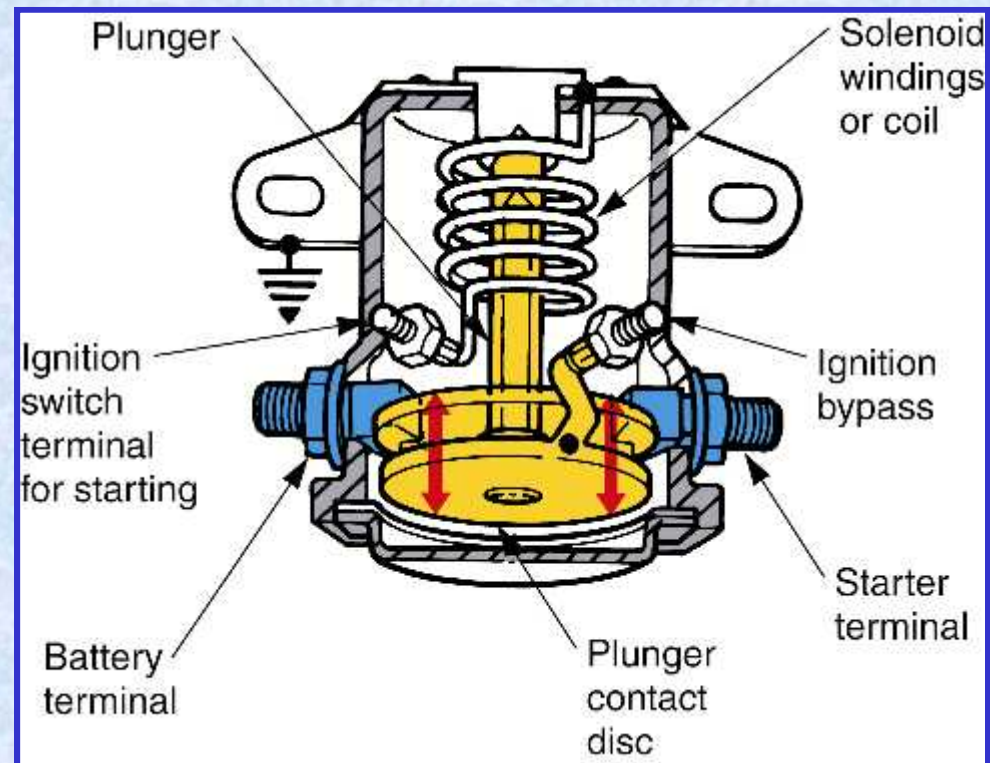
# Starter Solenoid


Plunger movement pulls the disc into contact with two battery terminals to activate the starter



# Solenoid Operation

- ❑ Low current flows through the windings
- ❑ The magnetic field pulls the solenoid plunger and disc toward the windings
- ❑ The disc touches both of the high-current terminals
- ❑ High current flows to the starter motor

# Solenoid Operation

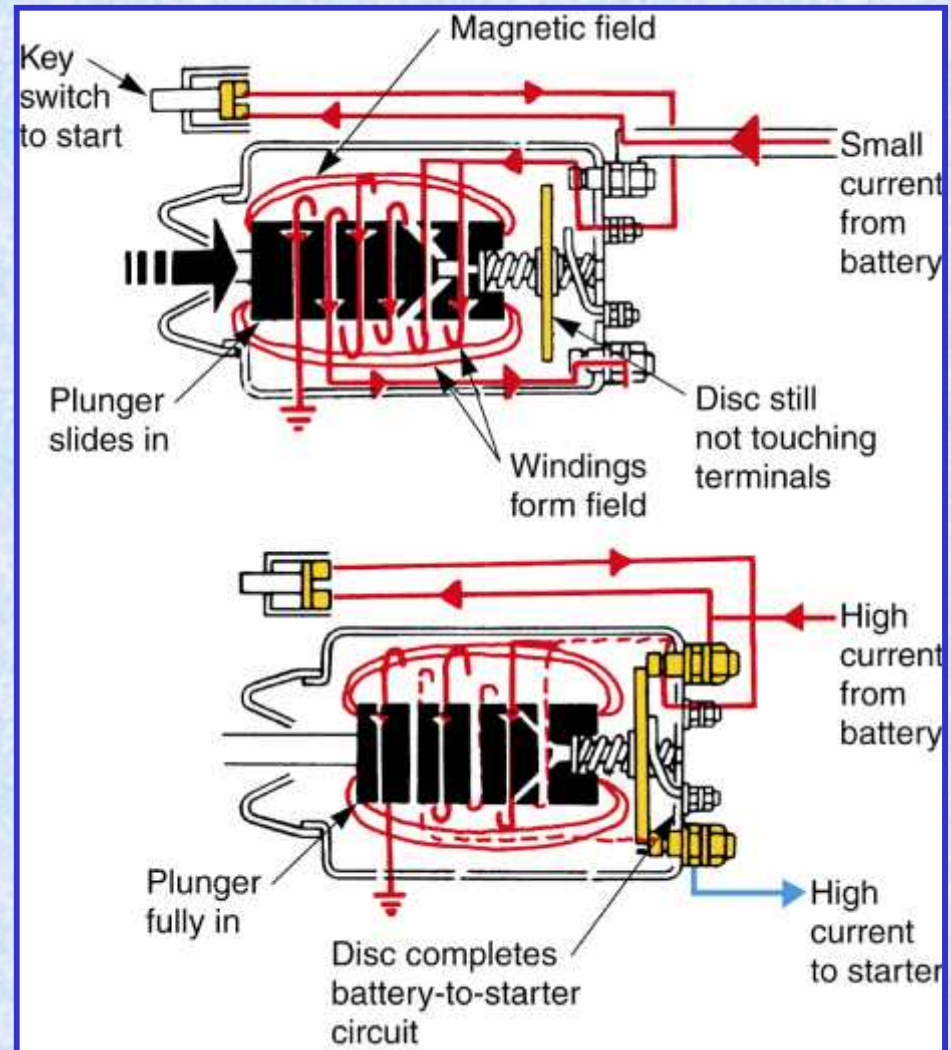

# Solenoid Functions


- ❑ Closes the battery-to-starter circuit
- ❑ Pushes the starter pinion gear into mesh with the flywheel ring gear
- ❑ Bypasses the resistance wire in the ignition circuit

# Starting Motor Construction

- Two types:
  - movable pole shoe starting motor
  - starter-mounted solenoid (starting motor with solenoid)

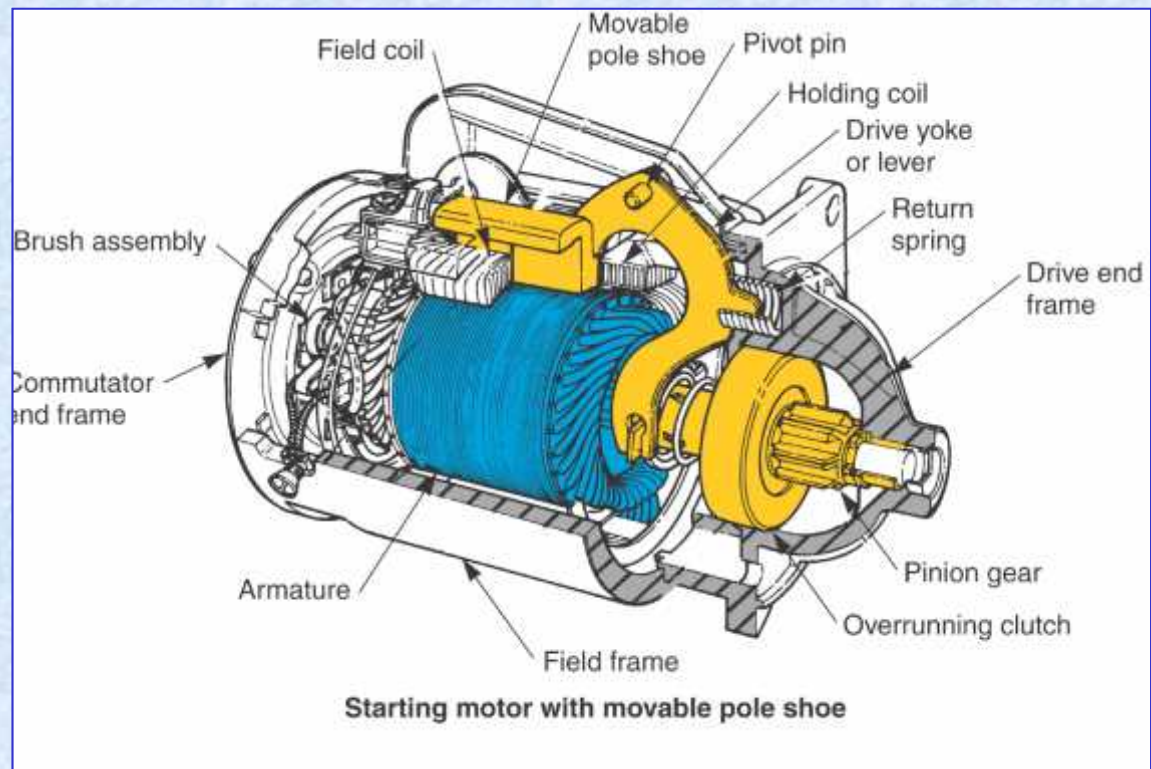
# Movable Pole Shoe Starting Motor

Uses a yoke lever to move the pinion gear into contact with the flywheel


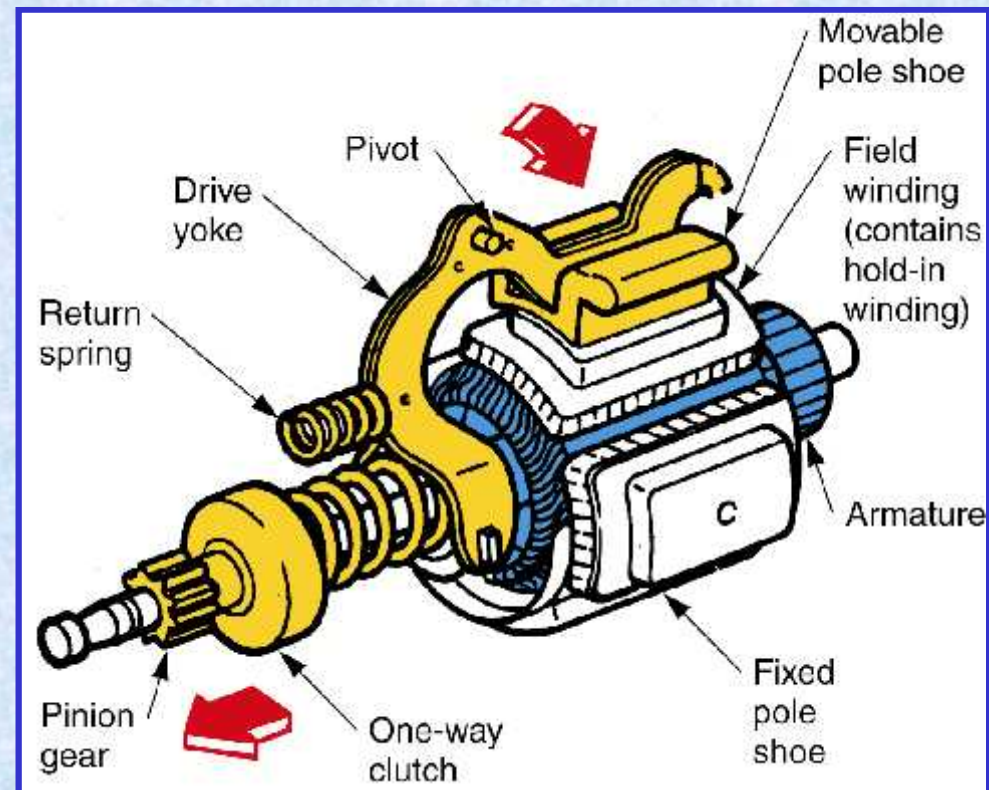
# Movable Pole Shoe Starting Motor


Magnetic field pulls the pole shoe downward, causing gear engagement as the armature starts to spin





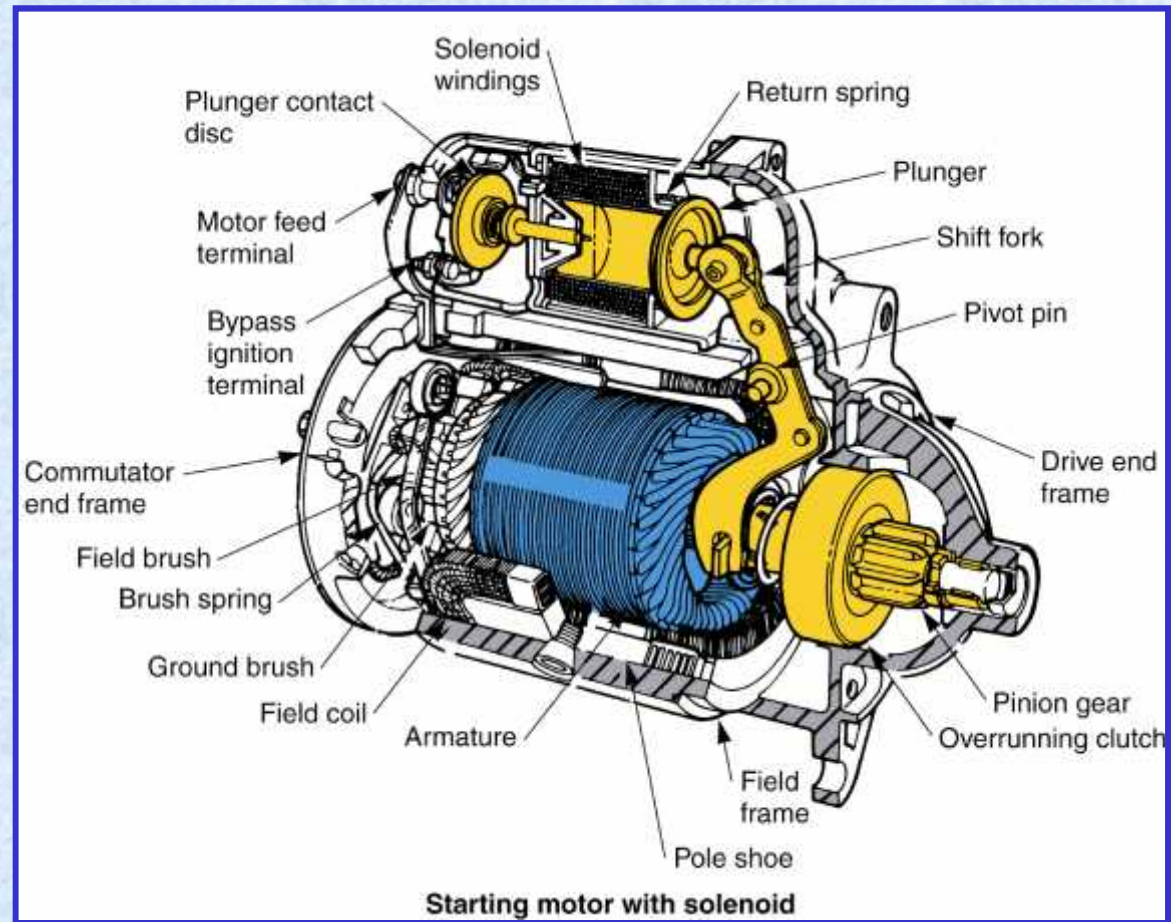
# Starter-Mounted Solenoid

Solenoid plunger moves a shift lever to engage the pinion gear



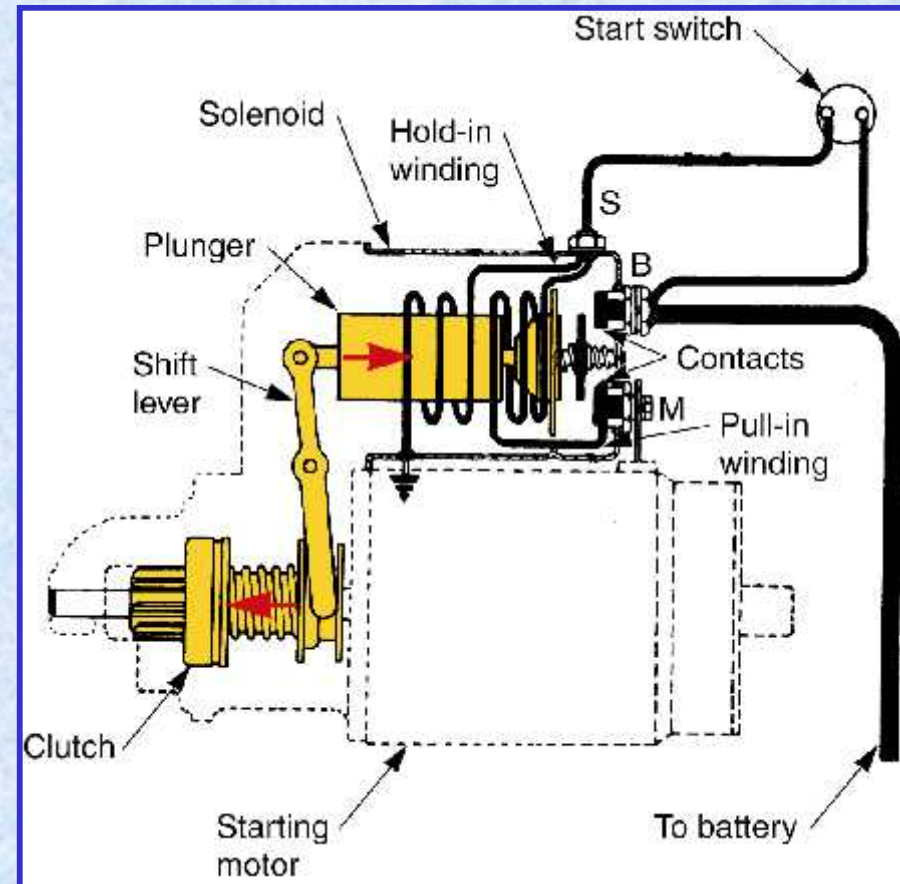
# Starter-Mounted Solenoid

Solenoid completes the battery-to-starter circuit




# Solenoid Operation

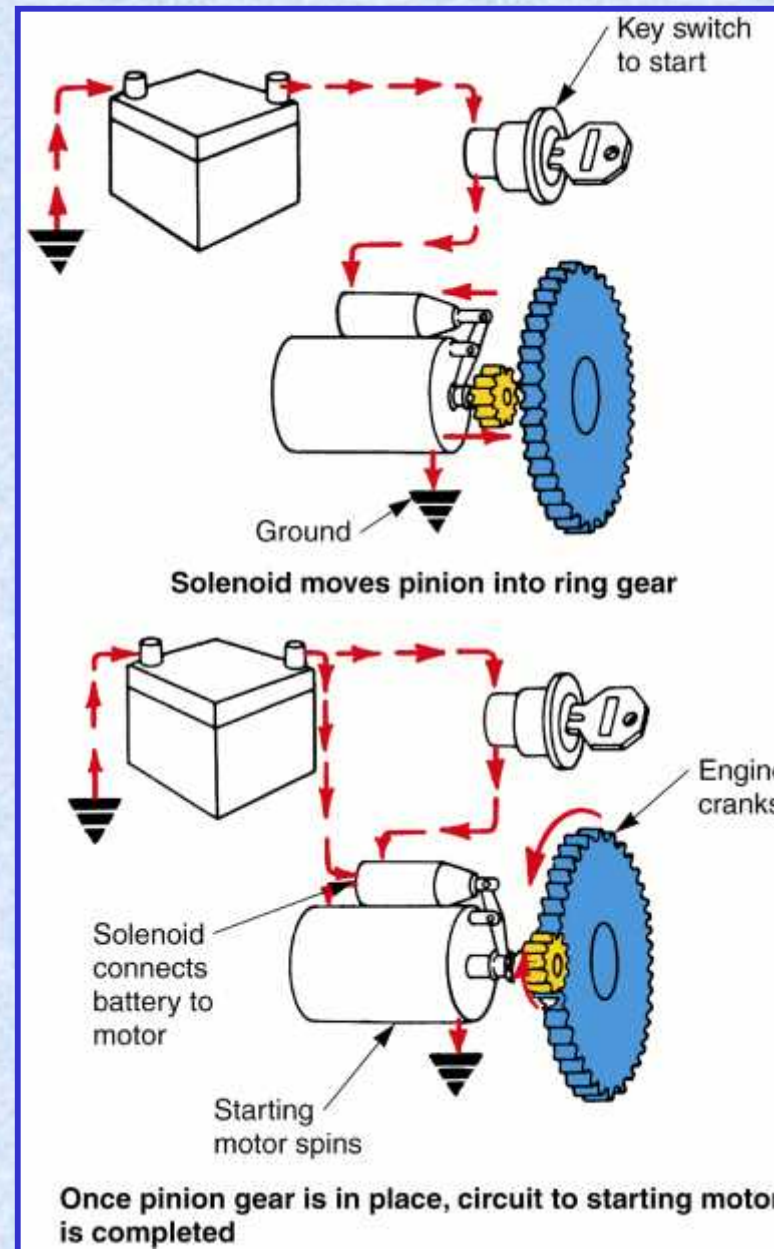
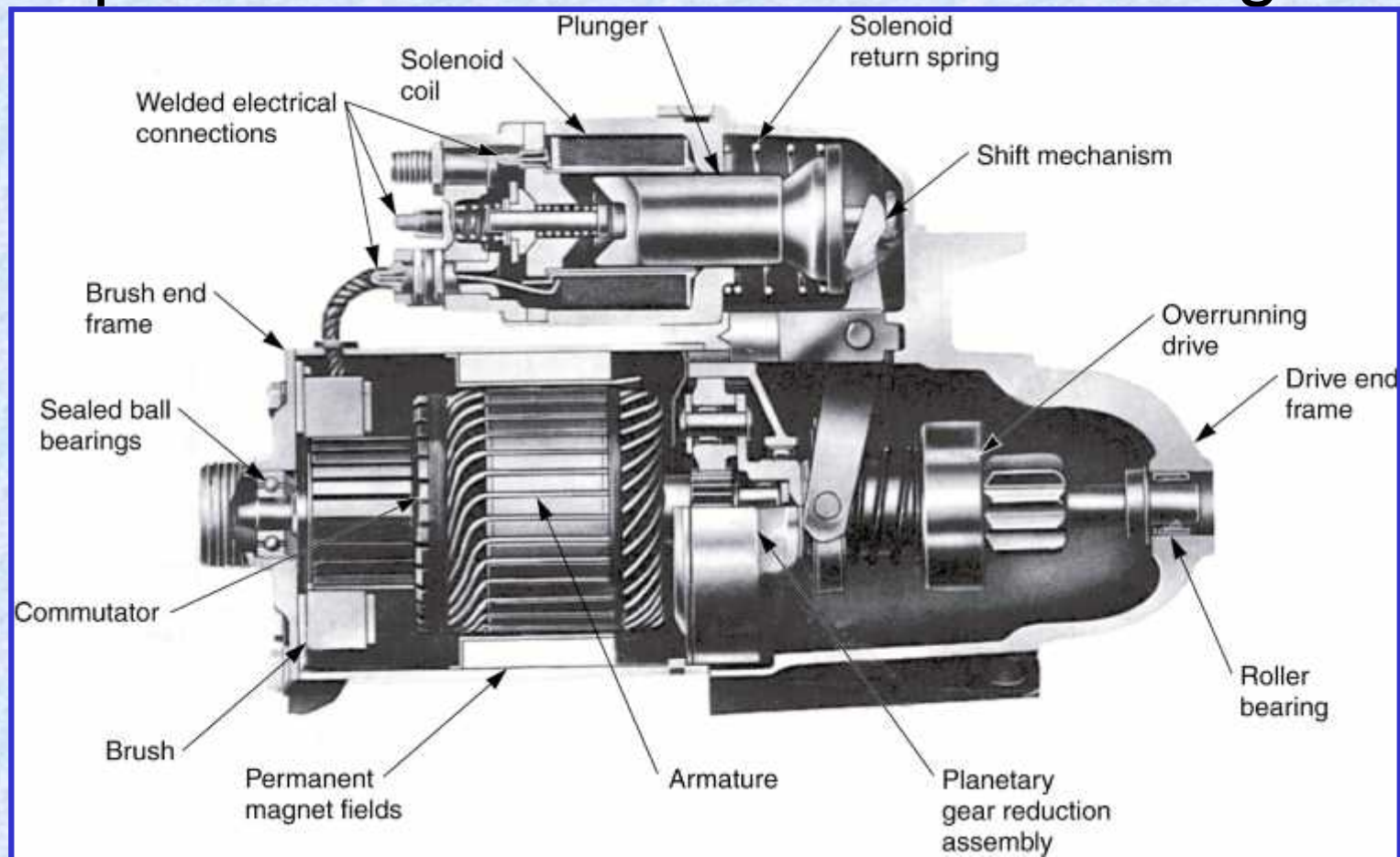
# Permanent-Magnet Starter

Uses special high-strength magnets in place of conventional field windings




# Starting Motor Torque

- ❑ A starting motor must produce high torque
- ❑ Difference in gear size between the small pinion and large flywheel ring gear increases turning torque

# Reduction Starter

Extra gears further increase torque

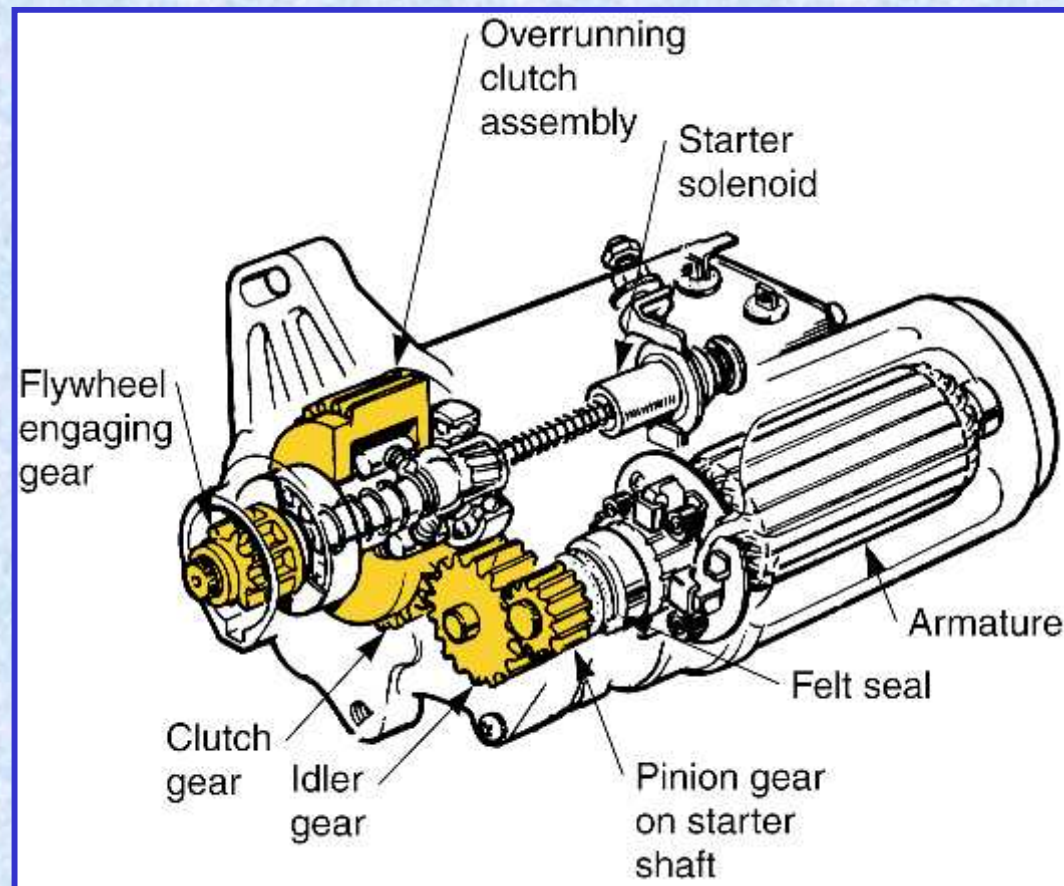


# Internal Motor Circuits

- Series-wound motor
- Shunt-wound motor
- Compound-wound motor
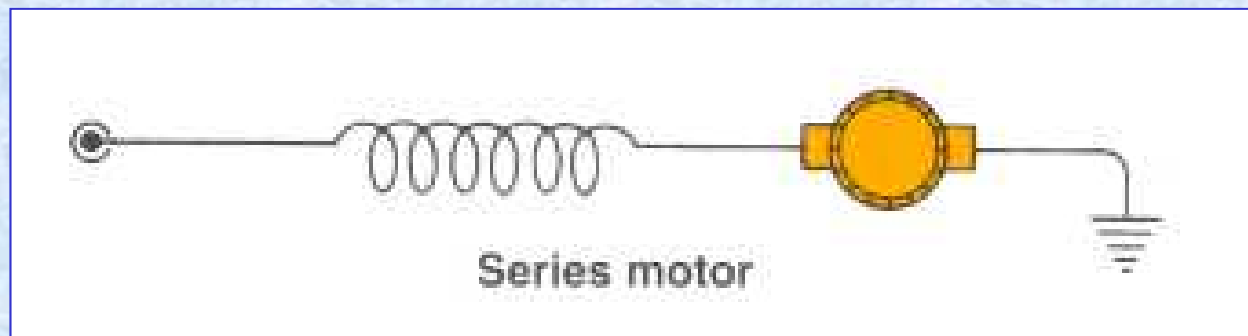
# Series-Wound Motor


Develops maximum torque at initial start-up and decreases as motor speed increases





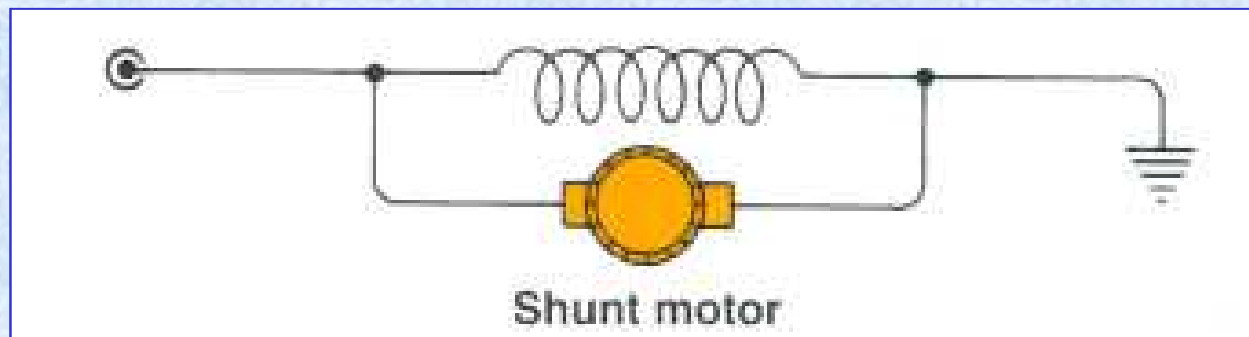
# Shunt-Wound Motor

Produces less starting torque but more constant torque at varying speeds


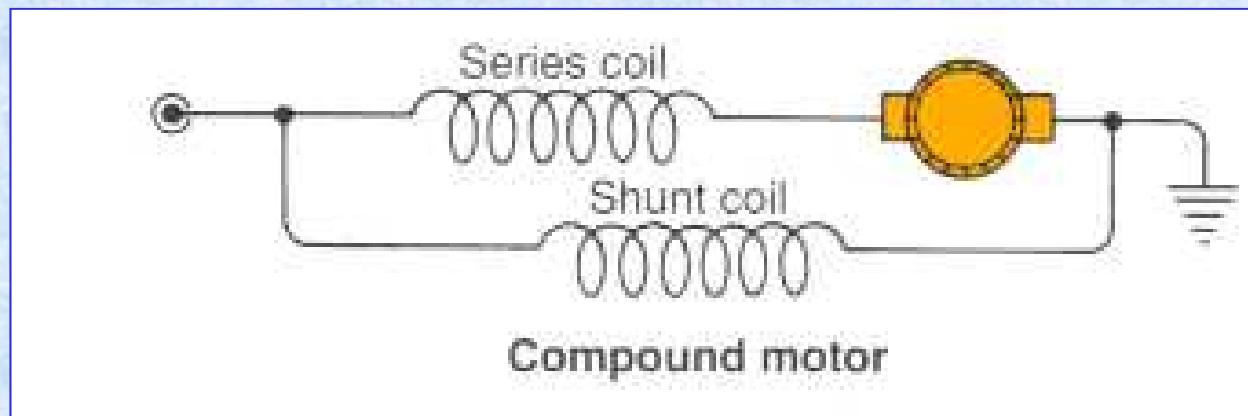
# Compound-Wound Motor

Has both series and shunt windings and produces good starting power and constant operating speed




# Neutral Safety Switch

- Prevents the engine from cranking unless the shift selector is in neutral or park
- Mounted on the shift lever or on the transmission
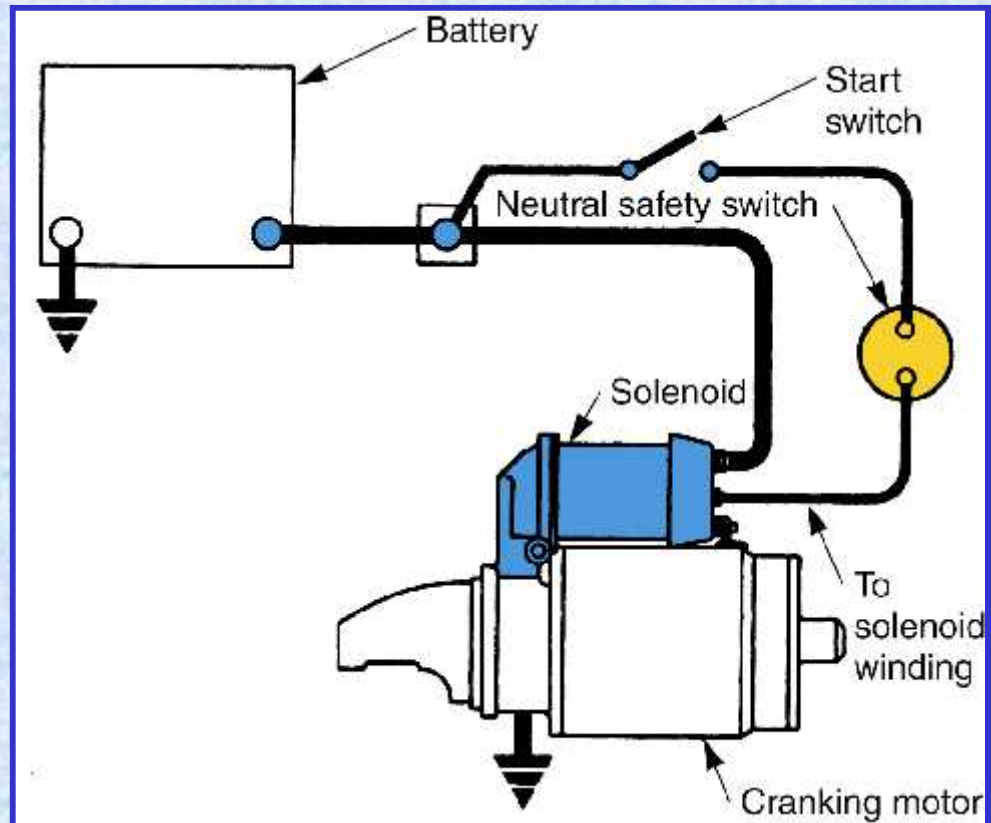
# Neutral Safety Switch

Wired in series with the starter solenoid



# Starter Relay

- ❑ Opens or closes one circuit by responding to an electrical signal from another circuit
- ❑ Uses a small current from the ignition switch to control a larger current through the starter solenoid
- ❑ Reduces the load on the ignition switch

# Starter Relay Operation

- ❑ Ignition switch is turned to “start”
- ❑ Current flows through the relay windings
- ❑ Magnetism closes the relay contacts
- ❑ Contacts complete the circuit to the solenoid windings, operating the starter motor

# Starting System Circuit

