


TRANSMISSION LINE THEORY

(TEM Line)

A uniform transmission line is defined as the one whose dimensions and electrical properties are identical at all planes transverse to the direction of propagation.

Circuit Representation of TL's

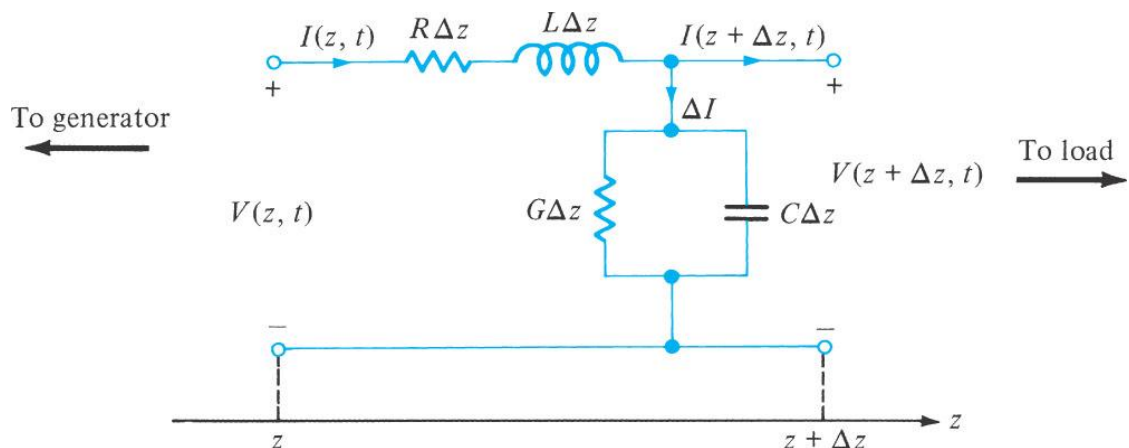A uniform TL may be modeled by the following circuit representation:



R: Series resistance per unit length of line (for both conductors (ohm/m)).

L: Series inductance per unit length of line (Henry/m).

G: Shunt conductance per unit length of line (mho/m).

C: Shunt capacitance per unit length of line (Farad/m).

The line is pictured as a cascade of identical sections, each of Δz long.

Since Δz can always be chosen small compared to the operating wavelength, an individual section of line may be analyzed using ordinary ac circuit theory. In the following analysis, we let $\Delta z \rightarrow 0$, so the results are valid at all frequencies (hence for any physical time variation).

Applying the Kirchhoff's voltage law to the line section gives:

$$v(z,t) = (R \Delta z) i(z,t) + (L \Delta z) \frac{\partial i(z,t)}{\partial t} + v(z + \Delta z, t)$$

Rearranging yields:

$$\frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

Letting $\Delta z \rightarrow 0$, we get,

$$\frac{\partial v(z, t)}{\partial z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

Now applying Kirchhoff's current law to the line section gives:

$$i(z, t) = (G \Delta z) v(z + \Delta z, t) + (C \Delta z) \frac{\partial v(z + \Delta z, t)}{\partial t} + i(z + \Delta z, t)$$

Rearranging yields:

$$\frac{i(z + \Delta z, t) - i(z, t)}{\Delta z} = -G v(z + \Delta z, t) - C \frac{\partial v(z + \Delta z, t)}{\partial t}$$

Letting $\Delta z \rightarrow 0$

$$\frac{\partial i(z,t)}{\partial z} = -G v(z,t) - C \frac{\partial v(z,t)}{\partial t}$$

Then the time domain TL or telegrapher equations are:

$$\frac{\partial v(z,t)}{\partial z} = -R i(z,t) - L \frac{\partial i(z,t)}{\partial t}$$

$$\frac{\partial i(z,t)}{\partial z} = -G v(z,t) - C \frac{\partial v(z,t)}{\partial t}$$

The solution of these equations, together with the electrical properties of the generator and load, allow us to determine the instantaneous voltage and current at any time t and any place z along the uniform TL.

Lossless Line: For the case of perfect conductors ($R=0$) and insulators ($G=0$), the telegrapher equations reduce to the following form:

$$\frac{\partial v(z,t)}{\partial z} = -L \frac{\partial i(z,t)}{\partial t}$$

$$\frac{\partial i(z,t)}{\partial z} = -C \frac{\partial v(z,t)}{\partial t}$$

$$\frac{\partial}{\partial z} \left(\frac{\partial v(z,t)}{\partial z} \right) = -L \frac{\partial}{\partial z} \left(\frac{\partial i(z,t)}{\partial t} \right)$$

$$-L \frac{\partial}{\partial t} \left(\frac{\partial i(z,t)}{\partial z} \right) = -L \frac{\partial}{\partial t} \left(-C \frac{\partial v}{\partial t} \right)$$

Or,

$$\frac{\partial^2 v(z,t)}{\partial z^2} - LC \frac{\partial^2 i(z,t)}{\partial t^2} = 0$$

$$\frac{\partial^2 i(z,t)}{\partial z} - LC \frac{\partial^2 i(z,t)}{\partial t^2} = 0$$

Wave equation's for voltage and current on a lossless TL.

Although real lines are never lossless, losslessness approximation for practical TL's is very useful.

TRANSMISSION LINES WITH SINUSOIDAL EXCITATION

We will only consider the sinusoidal steady-state solutions.

Transmission-Line Equations:

Under sinusoidal steady state conditions, the TL equations take the form:

$$\frac{dV(z)}{dz} = -(R + j\omega L)I(z)$$

$$\frac{dI(z)}{dz} = -(G + j\omega C)V(z)$$

Where $V(z)$ and $I(z)$ are voltage and current phasors.

The real sinusoidal voltage and current waveforms are obtained from:

$$v(z, t) = \text{Re} \left[V(z) e^{j\omega t} \right]$$

$$i(z, t) = \text{Re} \left[I(z) e^{j\omega t} \right]$$

Wave Propagation on a TL

The second order differential equations for $V(z)$ and $I(z)$ are:

$$\frac{d^2V(z)}{dz^2} - \gamma^2 V(z) = 0$$

$$\frac{d^2I(z)}{dz^2} - \gamma^2 I(z) = 0$$

where $\gamma = \alpha + j\beta = \left[(R + j\omega L)(G + j\omega C) \right]^{1/2}$

γ = complex propagation constant.

α = attenuation constant (Np/m).

β = phase constant (rad/m).