



Integrated Circuits Design by FPGA

م.م. أحمد مؤيد عبدالحسين جامعة الفرات الأوسط التقنية / الكلية التقنية الهندسية / نجف



VHDL Sequential Code

Objectives of this Lecture

- To understand what is the Sequential VHDL code.
- Also, this lecture is very important, for it allows a better understanding of where the parallel VHDL code or sequential VHDL code, as well as the consequences of using one or the other.
- To make comparison between IF, CASE, and WHEN statements.
- To indicate the main reasons behind **bad clocking**.

Contents of this Lecture

- Sequential VHDL code inside **Processes**\ Loop
- Sequential VHDL code IF vs. CASE
- Sequential VHDL code CASE vs. WHEN
- Bad Clocking

• As the name says, **LOOP** is useful when a piece of code must be instantiated several times.

• **PROCESSES**, **FUNCTIONS**, and **PROCEDURES** are the only sections of code that are executed sequentially. However, as a whole, any of these blocks is still concurrent with any other statements placed outside it .

• There are several ways of using **LOOP**, as shown in the syntaxes below. **FOR** / **LOOP**: The loop is repeated a fixed number of times.

```
[label:] FOR identifier IN range LOOP
 (sequential statements)
END LOOP [label];
```


• WHILE / LOOP: The loop is repeated until a condition no longer holds .

```
[label:] WHILE condition LOOP
 (sequential statements)
END LOOP [label];
```

• Example

WHILE (i < 10) LOOP WAIT UNTIL clk'EVENT AND clk='1'; (other statements) END LOOP;</pre>

• **EXIT**: Used for ending.

 

• NEXT: Used for skipping loop steps.

[label:] NEXT [loop_label] [WHEN condition];

Example with NEXT: In the example below, NEXT causes LOOP to skip one iteration when i = skip.

```
FOR i IN 0 TO 15 LOOP
   NEXT WHEN i=skip; -- jumps to next iteration
   (...)
END LOOP;
```

Example 6.8: Carry Ripple Adder


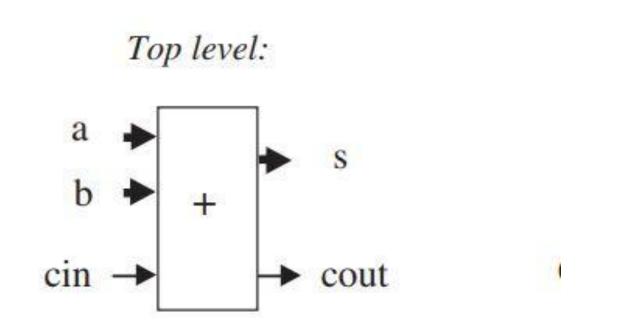


Figure 6.9 8-bit carry ripple adder of example 6.8

a b	cin	S	cout
00	0	0	0
01	0	1	0
10	0	1	0
11	0	0	1
00	1	1	0
01	1	0	1
10	1	0	1
11	1	1	1

Example 6.8: Carry Ripple Adder

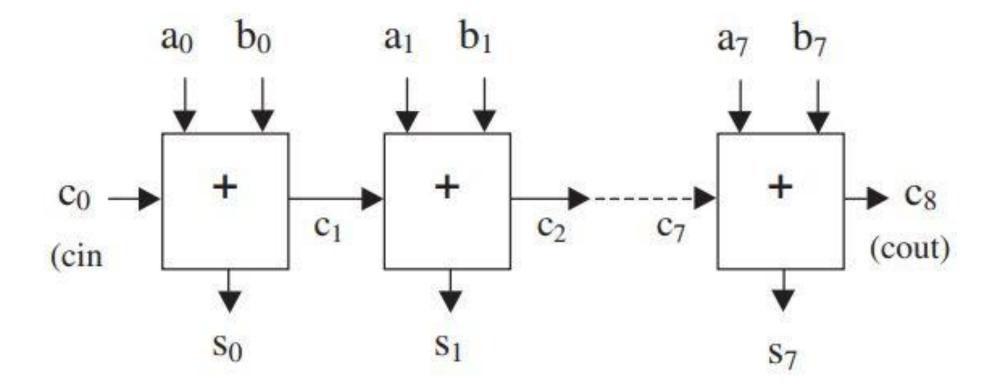

Each section of the latter diagram is a full-adder unit (section 1.4). Thus its outputs can be computed by means of:

 $s_j = a_j \text{ XOR } b_j \text{ XOR } c_j$

 $c_{j+1} = (a_j \text{ AND } b_j) \text{ OR } (a_j \text{ AND } c_j) \text{ OR } (b_j \text{ AND } c_j)$

```
----- Solution 1: Generic, with VECTORS
1
   LIBRARY ieee;
2
   USE ieee.std logic 1164.all;
3
    __________________________
  ENTITY adder IS
5
     GENERIC (length : INTEGER := 8);
6
     PORT ( a, b: IN STD LOGIC VECTOR (length-1 DOWNTO 0);
7
           cin: IN STD LOGIC;
8
           s: OUT STD LOGIC VECTOR (length-1 DOWNTO 0);
9
10
       cout: OUT STD LOGIC);
11 END adder;
12 -----
13 ARCHITECTURE adder OF adder IS
14 BEGIN
15
     PROCESS (a, b, cin)
16
        VARIABLE carry : STD LOGIC VECTOR (length DOWNTO 0);
17
     BEGIN
18
        carry(0) := cin;
19
        FOR i IN 0 TO length-1 LOOP
20
           s(i) <= a(i) XOR b(i) XOR carry(i);</pre>
21
          carry(i+1) := (a(i) AND b(i)) OR (a(i) AND
22
                        carry(i)) OR (b(i) AND carry(i));
23
        END LOOP;
24
        cout <= carry(length);</pre>
25
     END PROCESS;
26 END adder;
```

```
27 -----
```

 


Figure 6.10 Simulation results of example 6.8.

Example 6.8: Carry Ripple Adder

Example 6.9: Simple Barrel Shifter

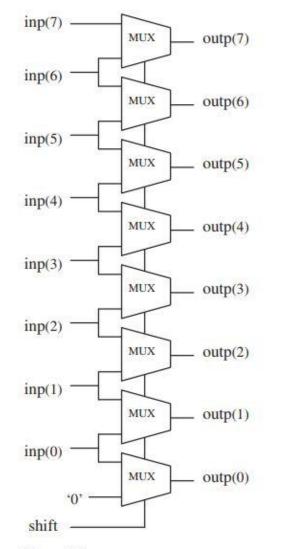


Figure 6.11 Simple barrel shifter of example 6.9.

Example 6.9: Simple Barrel Shifter

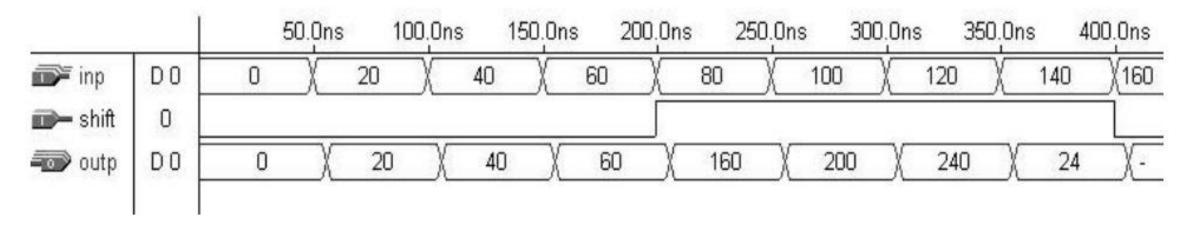


Figure 6.12 Simulation results of example 6.9.

```
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 ------
5 ENTITY barrel IS
6 GENERIC (n: INTEGER := 8);
7 PORT ( inp: IN STD_LOGIC_VECTOR (n-1 DOWNTO 0);
8 shift: IN INTEGER RANGE 0 TO 1;
9 outp: OUT STD LOGIC VECTOR (n-1 DOWNTO 0));
```

```
10 END barrel;
11
12 ARCHITECTURE RTL OF barrel IS
13 BEGIN
14
      PROCESS (inp, shift)
15
      BEGIN
16
         IF (shift=0) THEN
17
            outp <= inp;
18
         ELSE
19
            outp(0) <= '0';
20
            FOR i IN 1 TO inp'HIGH LOOP
21
             outp(i) \le inp(i-1);
22
            END LOOP;
23
         END IF;
24
      END PROCESS;
25 END RTL;
26
```

-	water a contract of the contract of the part of the
2	LIBRARY ieee;
3	USE ieee.std_logic_1164.all;
4	
5	ENTITY LeadingZeros IS
6	PORT (data: IN STD_LOGIC_VECTOR (7 DOWNTO 0
7	zeros: OUT INTEGER RANGE 0 TO 8);
8	END LeadingZeros;
9	
10	ARCHITECTURE behavior OF LeadingZeros IS

Example 6.10: Leading Zeros

11 BEGIN 12 PROCESS (data) 13 VARIABLE count: INTEGER RANGE 0 TO 8; 14 BEGIN 15 count := 0;16 FOR i IN data'RANGE LOOP 17 CASE data(i) IS WHEN '0' => count := count + 1; 18 19 WHEN OTHERS => EXIT; 20 END CASE; 21 END LOOP; 22 zeros <= count;</pre> 23 END PROCESS; 24 END behavior; 25

Example 6.10: Leading Zeros

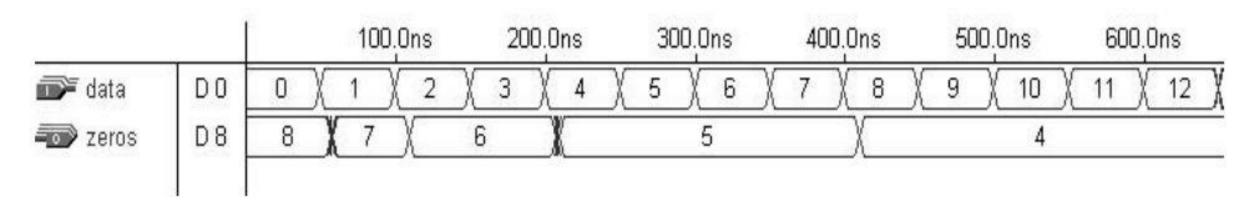


Figure 6.13 Simulation results of example 6.10.

Sequential VHDL code IF vs. CASE

Example: The codes below implement the same physical multiplexer circuit.

```
---- With IF: ------
IF (sel="00") THEN x \le a;
ELSIF (sel="01") THEN x<=b;
ELSIF (sel="10") THEN x<=c;
ELSE x<=d;
---- With CASE: ------
CASE sel IS
  WHEN "00" => x <= a;
   WHEN "01" => x \le b;
  WHEN "10" => x<=c;
   WHEN OTHERS => x<=d;
END CASE;
```

Sequential VHDL code WHEN vs. CASE

Example: From a functional point of view, the two codes below are equivalent.

```
---- With WHEN: -----
WITH sel SELECT
   x <= a WHEN "000",
          b WHEN "001",
          c WHEN "010",
          UNAFFECTED WHEN OTHERS;
 ---- With CASE: ------
CASE sel IS
   WHEN "000" => x<=a;
   WHEN "001" => x \le b;
   WHEN "010" => x <= c;
   WHEN OTHERS => NULL;
END CASE;
```

Sequential VHDL code WHEN vs. CASE

Table 6.1

Comparison between WHEN and CASE.


	WHEN	CASE
Statement type	Concurrent	Sequential
Usage	Only outside PROCESSES, FUNCTIONS, or PROCEDURES	Only inside PROCESSES, FUNCTIONS, or PROCEDURES
All permutations must be tested	Yes for WITH/SELECT/WHEN	Yes
Max. # of assignments per test	1	Any
No-action keyword	UNAFFECTED	NULL

PROCESS (clk) BEGIN

```
IF(clk'EVENT AND clk='1') THEN
    counter <= counter + 1;
ELSIF(clk'EVENT AND clk='0') THEN
    counter <= counter + 1;
END IF;
...
END PROCESS;</pre>
```

the compiler might display a message of the type **"signal does not hold value after clock edge"** or similar

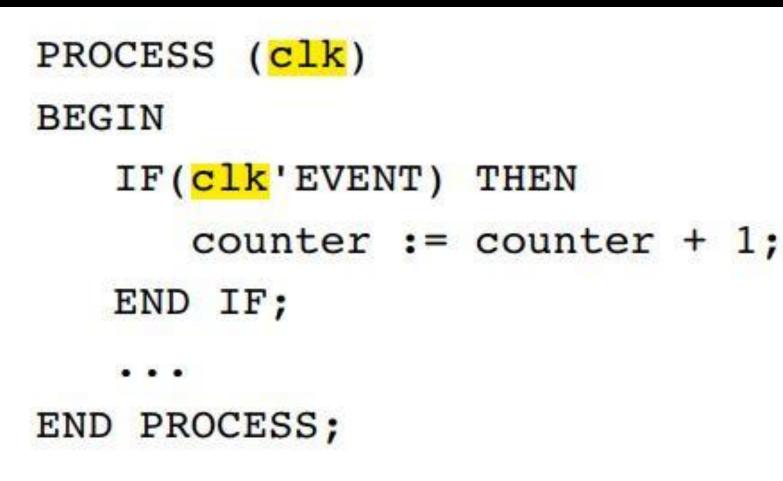• In this case, besides the messages already described, the compiler might also complain that the <u>signal counter is multiply driven</u>. In any case, compilation will be suspended.



In this case the compiler assumes a default test value (say "AND clk='1'") or issue a message of the type "clock not locally stable".

• Finally, if a signal appears in the sensitivity list, but does not appear in any of the assignments that compose the PROCESS, then it is likely that the compiler will simply ignore it.

```
PROCESS (clk)
BEGIN
counter := counter + 1;
...
END PROCESS;
```

However, a message of the type "ignored unnecessary pin clk" might be issued instead.



• The assignments will be attached to your class room.

End of lecture 6

Any Questions ?