



Integrated Circuits Design by FPGA

م.م. أحمد مؤيد عبدالحسين
جامعة الفرات الأوسط التقنية / الكلية التقنية الهندسية / نجف

Lecture 7

Multiplexer Circuit

Objectives of this Lecture

- To implement Multiplexer circuit using **WHEN** statement..
- To implement Multiplexer circuit using **CASE** statement.
- To indicate the difference between **WHEN** statement & **CASE** statement.

Contents of this Lecture

- Multiplexer project using **WHEN** statement.
- Multiplexer project using **CASE** statement

Multiplexer project using WHEN statement.


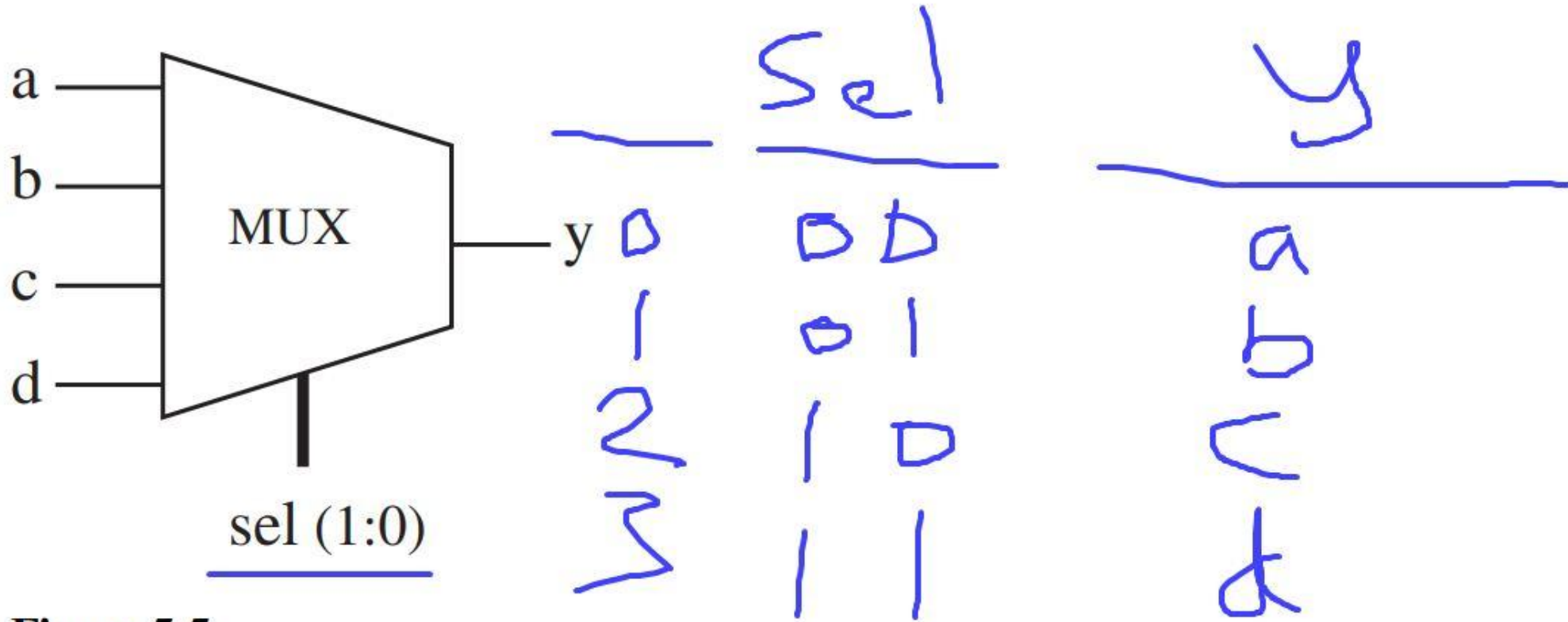


Figure 5.5
Multiplexer of example 5.2.

Multiplexer project using WHEN statement.

```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3  -----
4  ENTITY mux IS
5  PORT ( a, b, c, d: IN INTEGER RANGE 0 TO 100;
6         sel: IN STD_LOGIC_VECTOR (1 DOWNTO 0);
7         y: OUT INTEGER RANGE 0 TO 100);
8  END mux;
9  -----
10 ARCHITECTURE mux1 OF mux IS
11 BEGIN
12 y <= a WHEN sel="00" ELSE
13     b WHEN sel="01" ELSE
14     c WHEN sel="10" ELSE
15     d;
16 END mux1;
17 -----
```

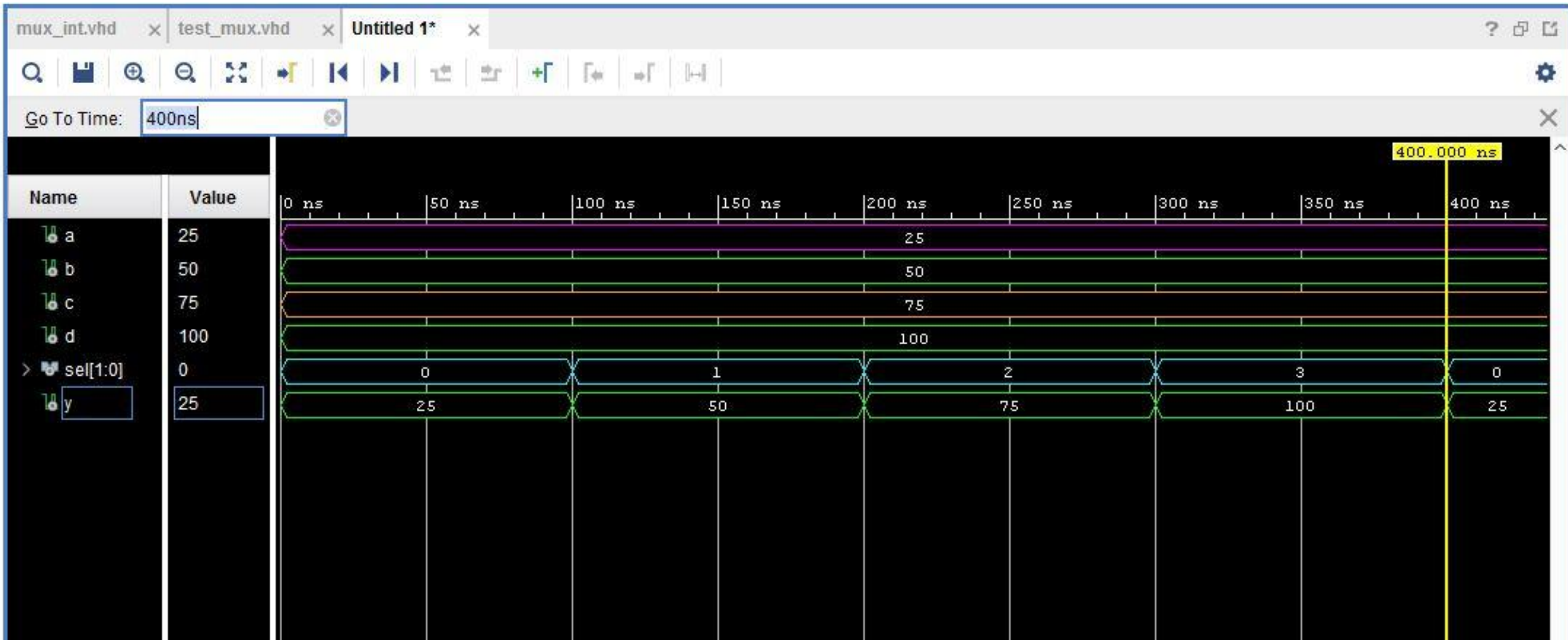
Multiplexer project using WHEN statement.



Multiplexer project using CASE statement.



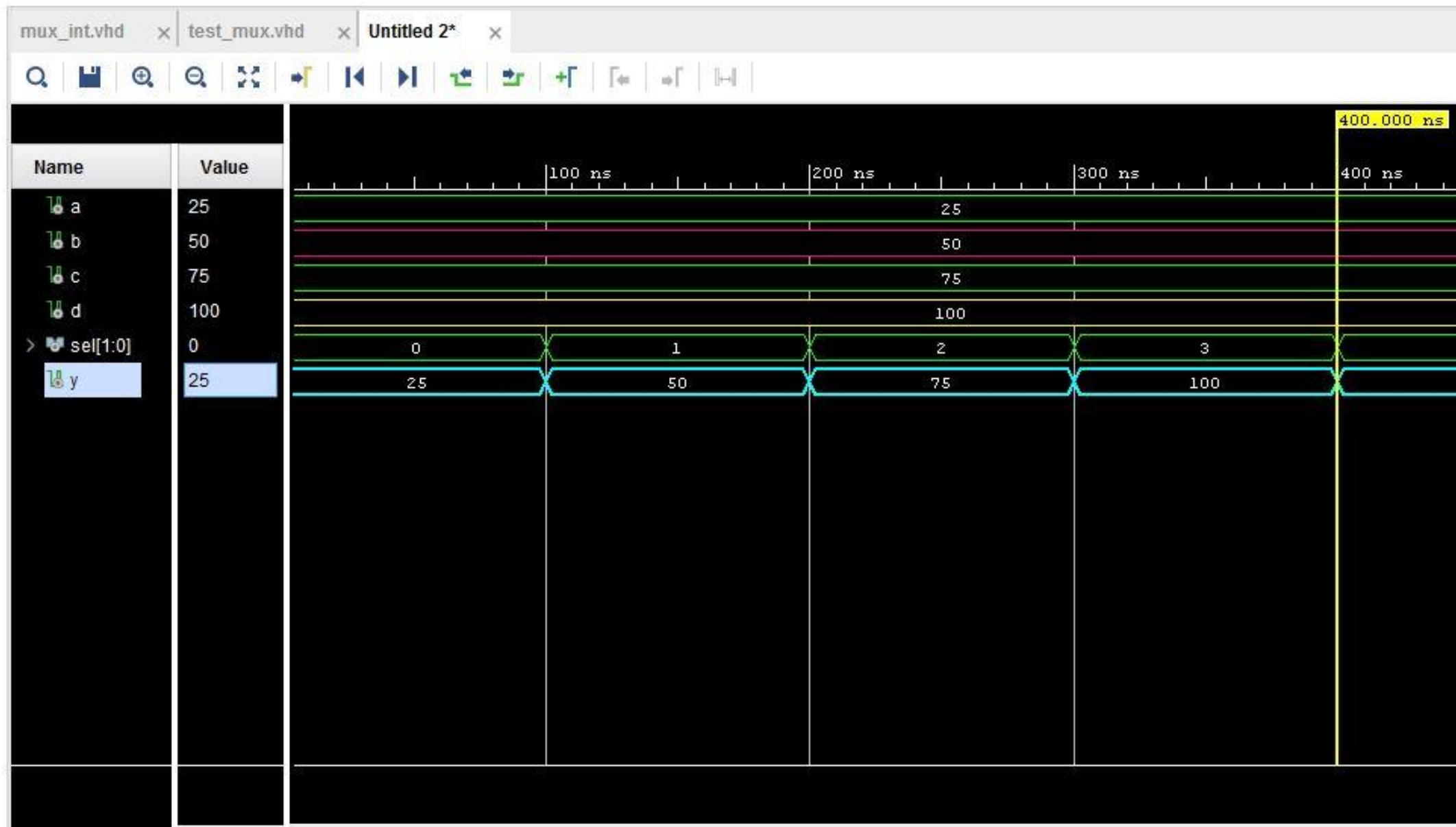Multiplexer project using CASE statement.



Assignments

- The assignments will be attached to your class room.

End of lecture 7

Any Questions ?