



جامعة الامارات
وزارة التعليم العالي والبحث العلمي
الى
وزارة التعليم العالي و البحث العلمي
جامعة الامارات الامريكية للتنمية
العلوم التقنية (المهندسية) / البنيات



قسم هندسة تقنيات الاتصالات

المرحلة الأولى

أمثلة الأصل الأول للعام الدراسي

٢٠١٧-٢٠١٦

متحان

شعبه فضلان العويس و الأمانة العامة



القسم : هندسة تقبيلات الاتصال
المرحلة : الأولى
المادة : الإلكترونيك
وقت الامتحان : ساعتان
التاريخ : ٢٠١٢ / ١١ / ٨

امتحان الفصل الأول للعام الدراسي ٢٠١٦ - ٢٠١٧

Note:

Answer all the questions

(24 degree)

Q1/Briefly answer only four items from the following:

1. Explain with drawing the conduction and valence bands of an insulators, semiconductors and conductors.
2. Describe the formation of depletion region.
3. What do you understand by the A.C & D.C resistance of a crystal diode.
4. Derive an expression for the efficiency of the half wave rectifier.
5. Describe the creation of electron-hole pairs in a silicon crystal.
6. Why are a semiconductors an insulators at ordinary temperature.

Q2>Select the correct choice for only five of the following statements (20 degree)


1. An addition of pentavalent impurities to a semiconductor creates
a) free electrons b) holes c) valence electrons d) bound electron
2. When a pure semiconductor is heated, its resistance is
a) Goes up b) goes down c) electrically neutral d) none of the above
3. In a semiconductor the conduction current is due to
a) Holes only b) free electrons only c) holes & electrons d) none of the above
4. The barrier voltage at a pn junction for germanium is about
a) 0.7 V b) 0.03 V c) 3 V D) none of the above
5. A pn junction acts as a.....
a) Controlled switch b) bidirectional switch c) unidirectional switch d) none of the above
6. The reverse saturation current I_s is exist at
a) No bias b) forward bias c) revers bias d) both c & b

Q3/ For the two figure bellow $R_L=100\Omega$, $V_{pri(rms)}=230$ V , $f_{in}=50$ Hz and $n=1/5$ assume silicon diode, Calculate the following for each network: (30 degree)


1)d.c voltage

2)PIV

3) F_{out}

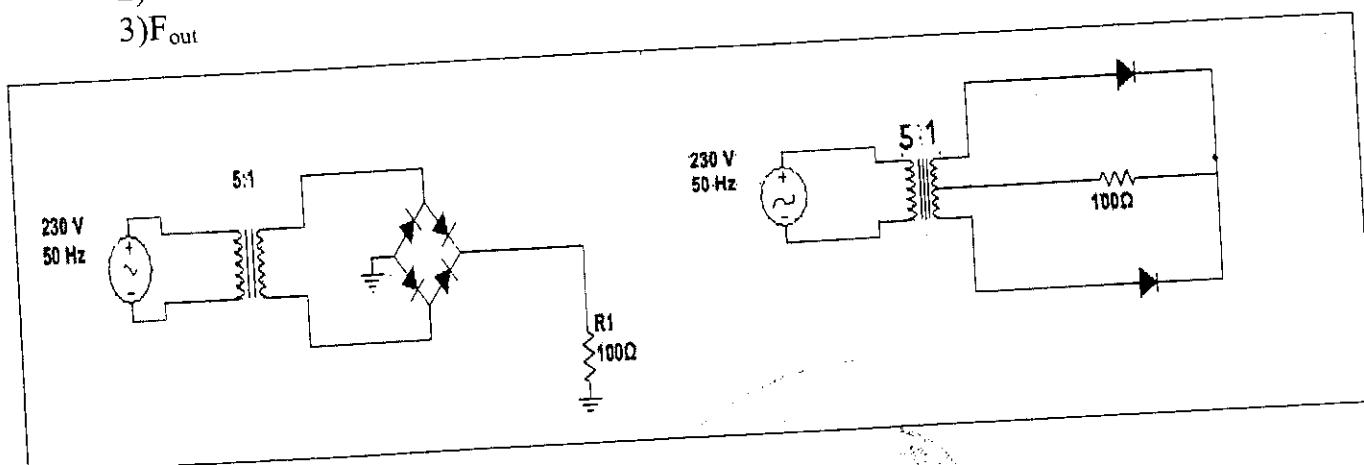

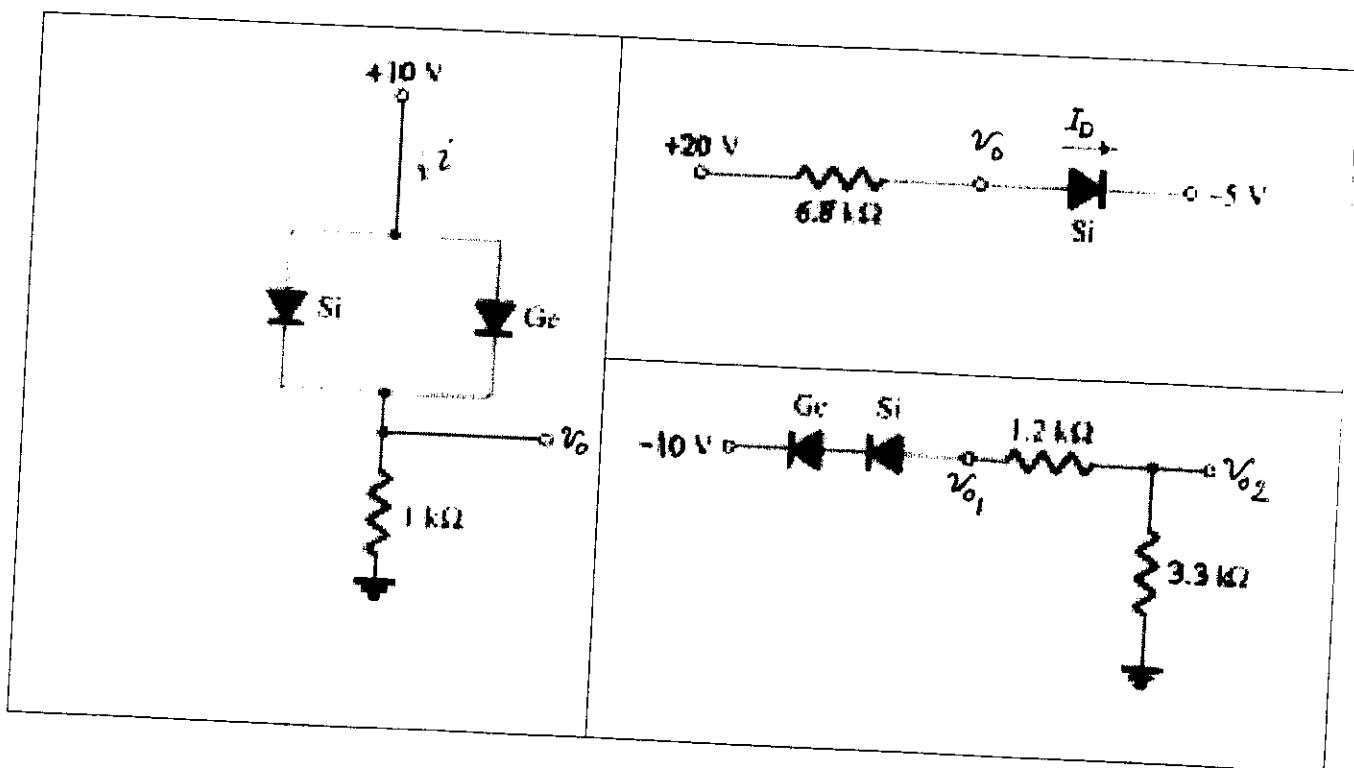Q4/ Determine V_o for two only of bellow networks: (26 degree)



مدرس المادة:
م.م احمد قائم



18/01/2017
رئيس القسم :
د. محمد حبيب

BEST WISHES

القسم : هندسة تقنيات الاتصالات
المرحلة : الاولى
المادة : حقوق الانسان
زمن الامتحان: ساعتان
التاريخ: 19 / 01 / 2017



جمهورية العراق
وزارة التعليم العالي والبحث العلمي
جامعة الفرات الأوسط التقنية
الكلية التقنية الهندسية / نجف

امتحان الفصل الأول - العام الدراسي 2016/2017

ملاحظة اجب عن جميع الاسئلة

س 1 / أ- وضح المقصود بالمصطلحات الآتية .:

1- الحق وفقاً للمفهوم الفردي 2- المقبرة الجماعية 3- الموطن . (15) درجة

ب- ضع كلمة صح امام العبارة الصحيحة وكلمة خطأ امام العبارة الخاطئة وصح الخطأ ان وجد . (10) درجة

1- ان الشخصية القانونية مقتصرة على الانسان الفرد فقط .

2- نص الدستور العراقي لسنة 2005 على ان الاسلام هو الدين الرسمي للدولة وهو المصدر الوحدى للتشريع .

3- اشترط دستور العراق لسنة 2005 عدم اخلال حرية الاجتماع والتظاهر السلمي بالنظام العام والأداب .

4- يقصد بالأسرة الرابطة التي تقوم بين الشخص ودولة ما وتجعله تابعاً لها .

5- نص الدستور العراقي لسنة 2005 تكفل الدولة حرية التعبير عن الرأي بكل الوسائل ، بما لا يخل بالنظام العام والأداب .

س 2/ تكلم عن مفهوم حقوق الانسان في سياق التطور التاريخي . (25) درجة

س 3/ عدد الحقوق الشخصية الواردة في دستور العراق لسنة 2005 ، واشرح اثنين ، على ان يكون الحق الاول من ضمنها . (25) درجة

س 4/ تعدد الاهليات احدى مميزات الشخصية الإنسانية ، ناقش ذلك . (25) درجة

19/01/2017

رئيس القسم
ليث وجيه عبدالله



مدرس المادة
حيدر عبد الجليل مهدي

First Course Examination 2016 - 2017

NOTE: Attempt Four Questions Only

- Q1:** (A) Derive torque equation for PMMC instruments. [Marks 10]
(B) Explain types of measurements errors. [Marks 15]
- Q2:** The following values were obtained from the measurements for a resistor in ohms:
220.2, 119.5, 221.1, 119.9, 220.0, 220.5, 119.8, 220.1, 220.4, and 119.8. Calculate
a. The arithmetic mean. [Marks 05]
b. The average deviation. [Marks 10]
c. The standard deviation. [Marks 10]
- Q3:** A recently calibrated digital voltmeter is used to read a voltage and it consistently yields 75 volts. Another meter in the lab is also used five times to measure the same voltage and following readings are obtained: 77, 75, 74, 76, 77. For the second meter, Find the absolute accuracy, relative accuracy and percentage accuracy. [Marks 25]
- Q4:** Design an Ayrton shunt (indirect method) to provide an ammeter with current ranges 1A, 5A and 10A. A basic meter with an internal resistance of (60Ω) and half scale deflection current of ($60 \mu A$) is to be used. [Marks 25]
- Q5:** A basic D'Arsonval meter with an internal resistance $R_m = 100 \Omega$ and a full scale current of $1mA$, is to be converted into a d.c. voltmeter with ranges of 0-10 V, 0-50V, 0-100V. Find the values of the multiplier resistances [Marks 25]

Good Luck

Examiner

Abdullah Al-M. Khash

I-1

22/01/2017

Department Head

Laith Wajeeh



Q1: Obtain the equivalent resistance of the circuits in Fig.1.

(30 Marks)

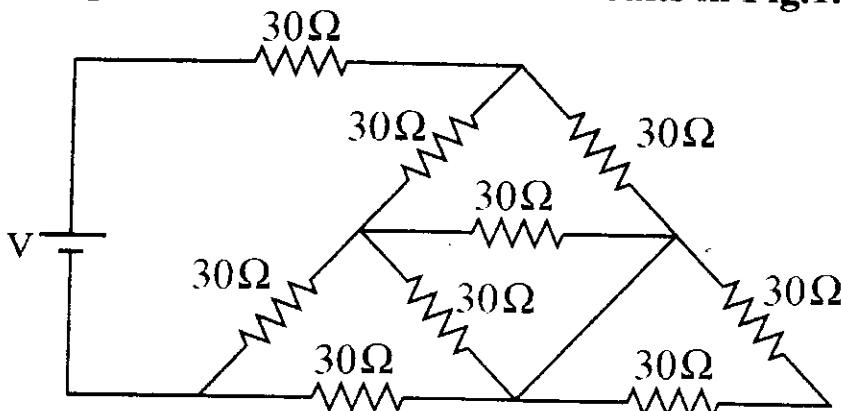


Fig.1

Q2: Find (I) in the circuit of Fig.2 using source transformation.

(30 Marks)

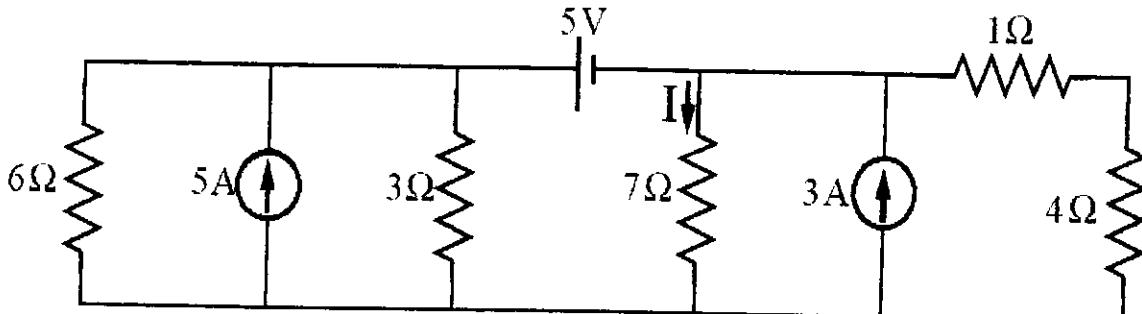


Fig.2


Q3:-

A- : An electrical resistive load takes a current of 12A from a 220V supply.

Calculate the cost of electricity if the equipment is used for 40 hours and the cost of 1kWh of energy is 100 dinars. (10 marks)

B- : A coil of Copper wire has a cross-sectional area of 0.8mm^2 and a length of 1600m. Find the resistance of the coil and the power consumed when the coil is connected across 100V DC supply. (Take the resistivity of copper as $0.02 \times 10^{-6} \Omega\cdot\text{m}$). (10 marks)





(تكملاً للأسئلة في الصفحة التالية)

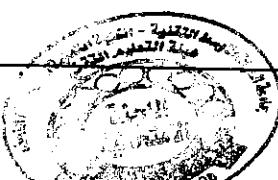

Q4: عليها (element), (branch), (node) لاحظة: يجب رسم جميع الدوائر الكهربائية في الدفتر الامتحاني وتحديد كل



A- Determine the number of elements, branches, nodes and essential nodes , the circuits shown below.

(10 marks)

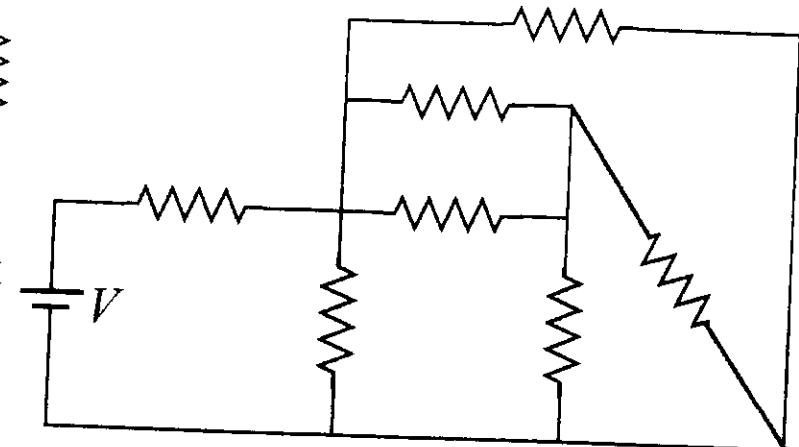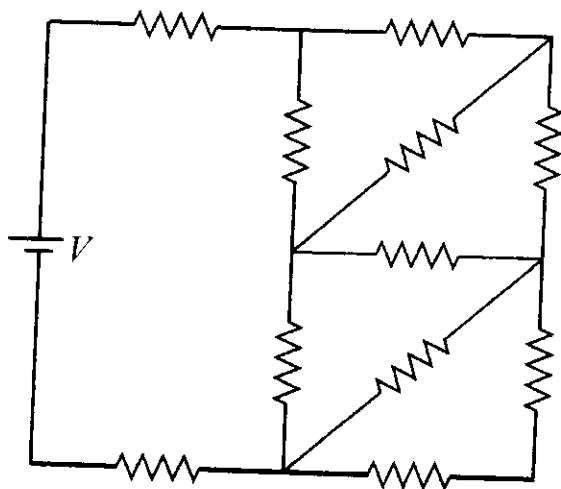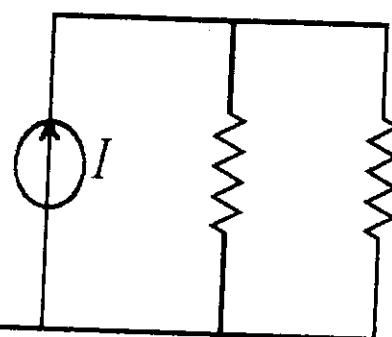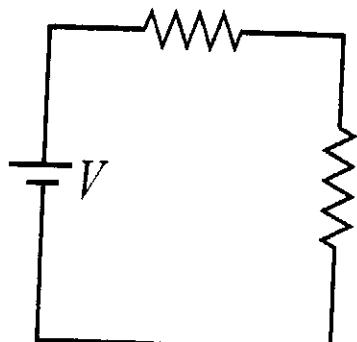

B- Determine the number of meshes and loops in the circuits shown below.

(10 marks)

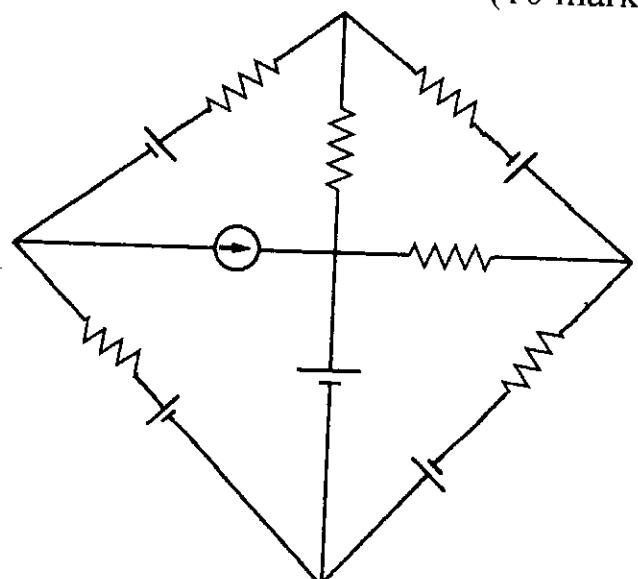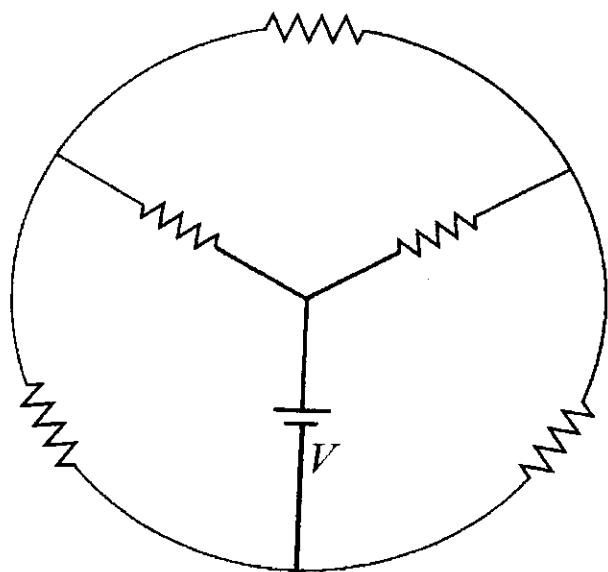

بالتفوق والنجاح

24/01/2017

رئيس القسم
ليث وجيه عبد الله



مدرس المادة
د. ناصر حسين سلمان

القسم : هندسة تقنيات الاتصالات
المرحلة : الاولى / اولى
المادة : الرياضيات
زمن الامتحان : ساعتان
التاريخ : 29 / 01 / 2017




امتحان الفصل الأول - العام الدراسي 2016/2017

Q1: Find all properties and graph for the following trigonometric functions: 20 M

$$1. \quad y = -\frac{3}{2} \cos\left(2x + \frac{\pi}{3}\right) - \frac{1}{2}$$

$$2. \quad y = 4 \sin(-2\pi x + \pi)$$

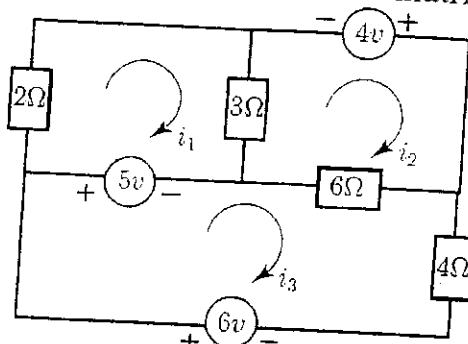Q2: In the circuit shown, write the loop equations and put them as a matrix includes currents (i_1, i_2, i_3) in their loops. 10 M



Q3: Perform the indicated operations in the following Problems, if possible. 20 M

$$1- \begin{bmatrix} 4 & 0 \\ -2 & 3 \\ 8 & 1 \end{bmatrix} + \begin{bmatrix} -1 & 2 \\ 0 & 5 \\ 4 & -6 \end{bmatrix}$$

$$2- \begin{bmatrix} 4 & 0 \\ -2 & 3 \\ 8 & 1 \end{bmatrix} + \begin{vmatrix} -1 & 0 & 4 \\ 2 & 5 & -6 \end{vmatrix}$$

$$3- \left(\begin{bmatrix} 1 & -1 \\ 0 & 2 \end{bmatrix} \begin{bmatrix} 3 & 0 \\ 5 & -1 \end{bmatrix} \right)^T$$

$$4- \begin{bmatrix} 2 & 0 & -1 & 3 \\ 1 & -1 & 2 & -2 \end{bmatrix} \begin{bmatrix} 1 & 1 & -8 \\ 1 & 0 & 0 \\ 0 & 5 & 2 \\ -2 & 8 & -1 \end{bmatrix}$$

Q4: Use Cramer's rule to solve the system: 20 M

$$\begin{aligned} x_1 - 2x_2 + x_3 &= 3 \\ 2x_1 + x_2 - x_3 &= 5 \\ 3x_1 - x_2 + 2x_3 &= 12. \end{aligned}$$

رئيس القسم
ليث وجيه عبدالله

29/01/2017

مدرس المادة



Q5: find the derivative for the following functions: 30 M

1- $y = 10 \tan(20x)$ 2- $f(x) = 10 \cos^3(4x)$

3- $f(x) = \frac{5x^2 + 7x}{x^2 + 2}$ 4- $f(x) = e^x(x^2 + 3)(x^3 + 4)$

5- $f(x) = \ln(5x^2 + 9)^3$



(2-2)

القسم : هندسة تقنيات الاتصالات
المرحلة : الاولى /
المادة: تطبيقات الحاسوب
زمن الامتحان: ساعتان
التاريخ: ٣١ / ٠١ / ٢٠١٧



امتحان الفصل الأول - العام الدراسي ٢٠١٦/٢٠١٧

Answer all the questions

Q1 /A/What is the differences between Inputs / Outputs units? (15Marks)

Q1 /B/Write with short notes about types of Ms-Dos System Commands? (10Marks)


Q2 / Fill in the blanks. (25Marks)

- 1- Memory space is measured by bit and byte that's mean bit equal ----- Byte.
- 2- There are two basic of component in CPU-----and-----
- 3- The memory is dividing into two parts ----- and-----.
- 4- The operating system Ms-Dos stored five attributes to each file ----- , -----, -----, ----- and -----.
- 5- There are two types of files in Ms-Dos system are ----- and ----- .

Q3/Write about the features that distinguish between Ms-Dos System and Windows. (25Marks)

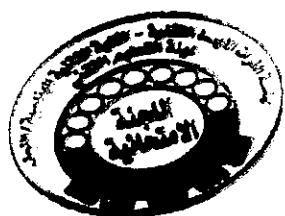Q4 /Use Ms-Dos system Commands to answer the following (25Marks)

- 1- Create a directory on the Desktop named Communication Engineer with file Tele.txt
- 2- Rename the directory Communication Engineer to IT Engineer
- 3- Rename the file Tele.txt to Tele.doc
- 4- Displayed all files in IT Engineer.
- 5- Copy directory IT Engineer to (D: drive).
- 6- Delete Tele.doc
- 7- Remove a Directory IT Engineer.
- 8- Display the date & time after delete the directory.



Best Wishes

رئيس القسم
ليث وجيه عبدالله

٣١ / ٠١ / ٢٠١٧

مدرس المادة
ياسر عبدالزهير